

---

# Coupling of numerical and symbolic MOR techniques



**Fraunhofer** Institut  
Techno- und  
Wirtschaftsmathematik



---

Workshop  
"Model Reduction for Circuit Simulation",  
October 30-31, 2008, Hamburg, Germany

Oliver Schmidt

---

# Overview

Motivation for symbolic methods

Symbolic techniques

Hierarchic systems

Workflow for exploitation of the hierarchy

# Symbolic Analysis

## Folded-Cascode OpAmp

### Problem


What causes resonance at 10 MHz?

### Classic approach

parameter variations and numerical simulation failed because of huge number of parameters
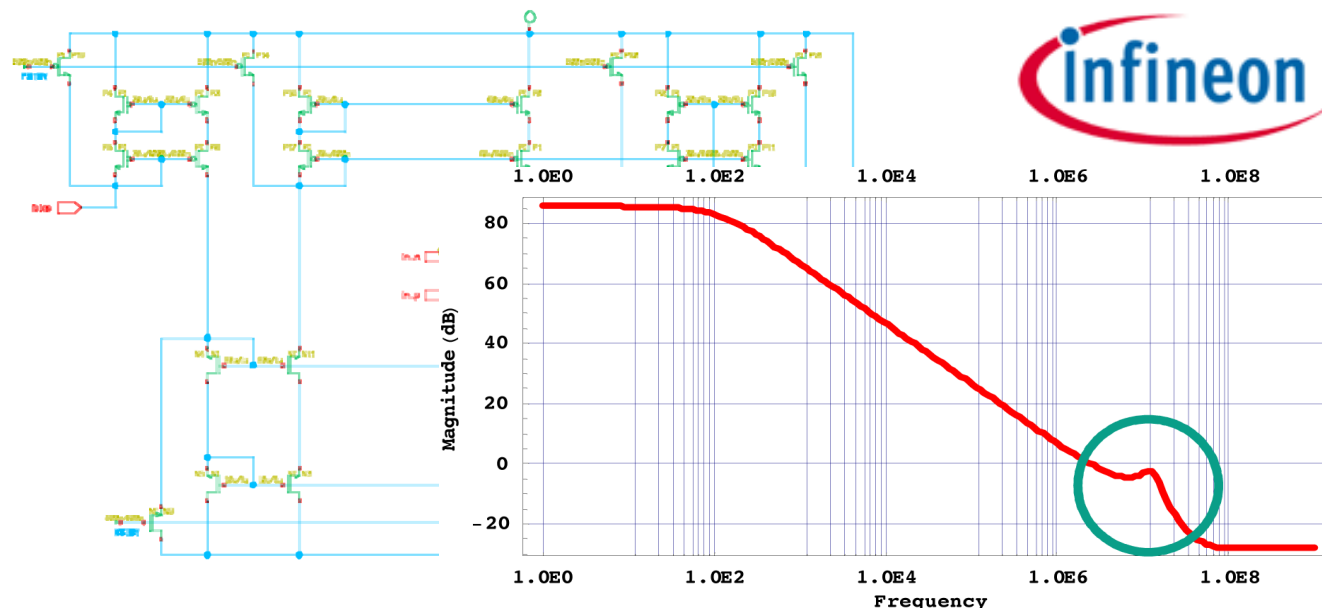
### Symbolic analysis

calculation of the transfer function and derivation of a symbolic formula for the resonance frequency



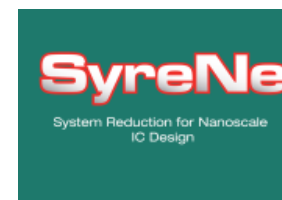
### Complexity problem

exact symbolic transfer function consists of more than  $5 \cdot 10^{19}$  terms  
printed: paper stack with a height of  $15 \cdot 10^9$  miles  
differential order: 19



Fraunhofer Institut  
Techno- und  
Wirtschaftsmathematik



# Symbolic Analysis

## Folded-Cascode OpAmp

### Problem


What causes resonance at 10 MHz?

### Classic approach

parameter variations and numerical simulation failed because of huge number of parameters
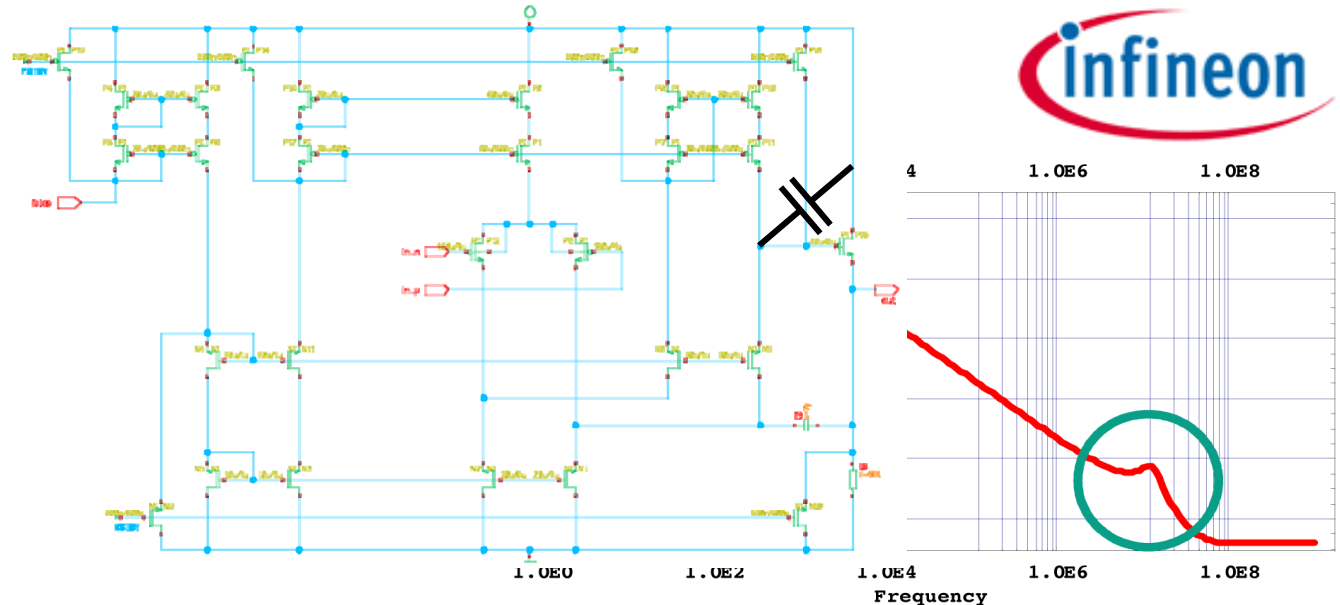
### Symbolic analysis

calculation of the transfer function and derivation of a symbolic formula for the resonance frequency



Complexity problem  $\Rightarrow$  symbolic approximation

$$s_{p1,2} = - \frac{(CC0 + CL) gm\$MN6}{2 CC0 CL} \pm \sqrt{\frac{Cgs\$MP15 gm\$MN6 (Cgs\$MP15 (CC0 + CL)^2 gm\$MN6 - 4 CC0^2 CL gm\$MP15)}{2 CC0 Cgs\$MP15 CL}}$$



# Symbolic Analysis

## Folded-Cascode OpAmp

### Problem


What causes resonance at 10 MHz?

### Classic approach

parameter variations and numerical simulation failed because of huge number of parameters
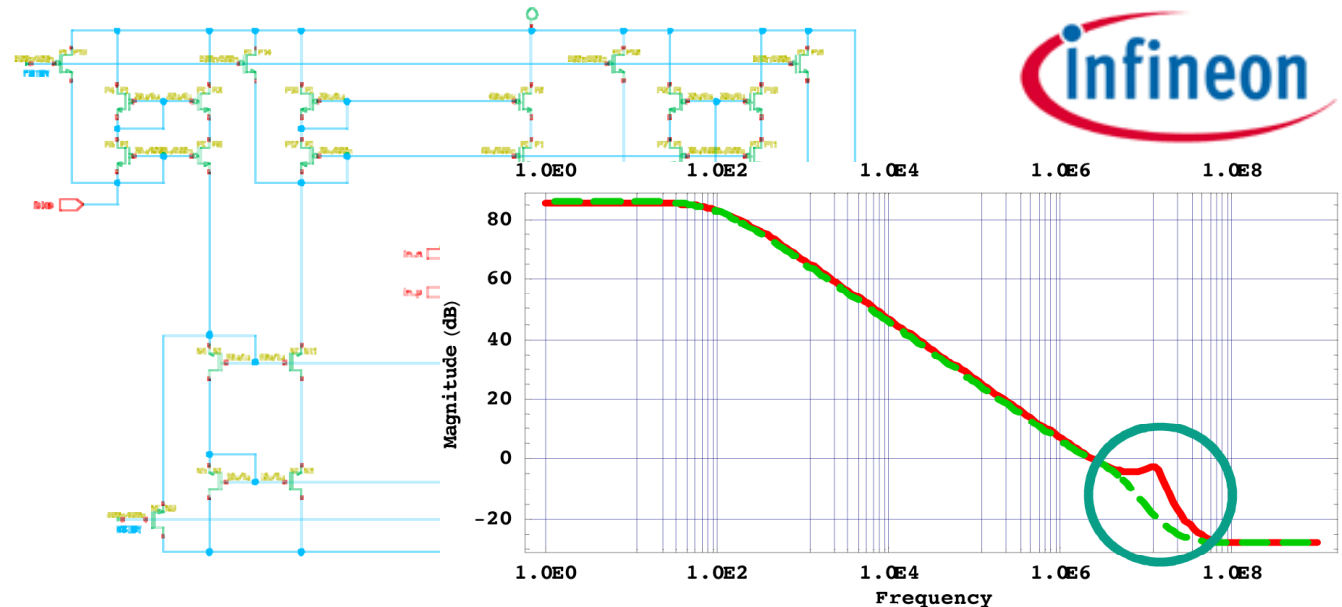
### Symbolic analysis


calculation of the transfer function and derivation of a symbolic formula for the resonance frequency



Complexity problem  $\Rightarrow$  symbolic approximation

$$s_{p^{1,2}} = - \frac{(CC0 + CL) gm\$MN6}{2 CC0 CL} \pm \sqrt{\frac{Cgs\$MP15 gm\$MN6 (Cgs\$MP15 (CC0 + CL)^2 gm\$MN6 - 4 CC0^2 CL gm\$MP15)}{2 CC0 Cgs\$MP15 CL}}$$

# Numerical Validation

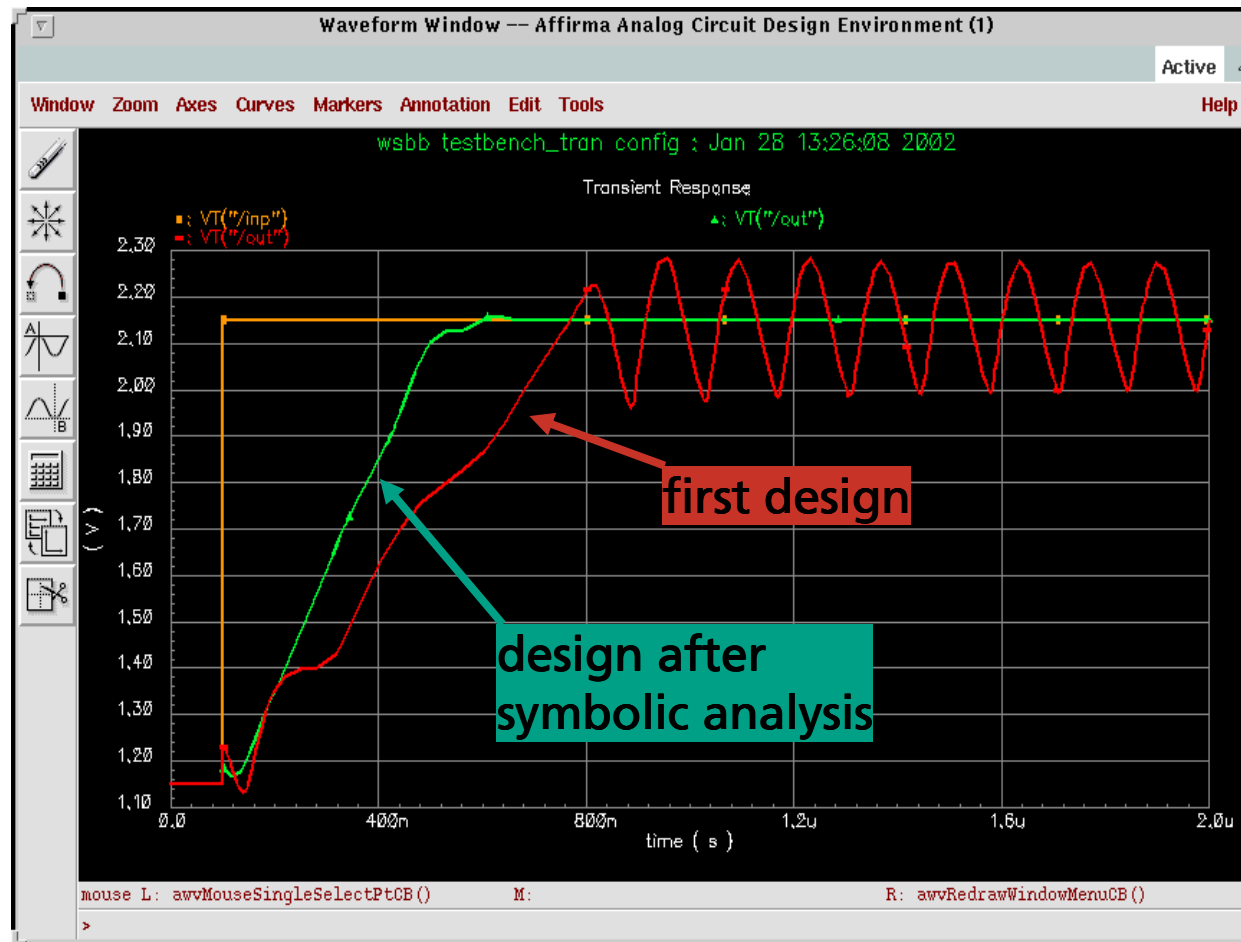

Fraunhofer Institut  
Techno- und  
Wirtschaftsmathematik



---

# Overview

Motivation for symbolic methods


Symbolic techniques

Hierarchic systems

Workflow for exploitation of the hierarchy

# Nonlinear Symbolic Analysis

netlist description

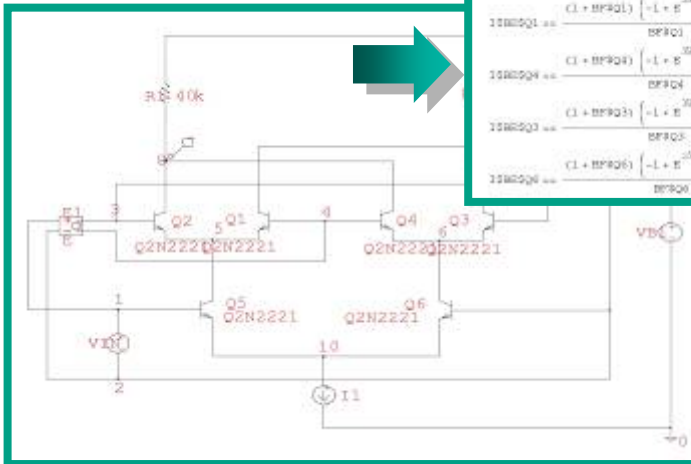

original DAE system

$$\begin{cases} I_{B1} - I_{B2} + I_{B3} + I_{B4} - I_{B5} - I_{B6} = 0, \\ I_{C1} + I_{C2} + I_{C3} + I_{C4} + I_{C5} + I_{C6} = 0, \\ \dots \end{cases}$$

simplified DAE system

$$\begin{cases} I_1 - E \frac{V_{IN} - V_{S10}}{V_T} - \frac{V_{S10}}{V_T} I_{SSQ5} - E \frac{V_{S10}}{V_T} I_{SSQ6} = 0, \\ -E \frac{V_{B1} - E_1 V_{IN} - V_{S5}}{V_T} I_{SSQ1} - E \frac{V_{S5}}{V_T} I_{SSQ2} + E \frac{V_{IN} - V_{S10}}{V_T} I_{SSQ5} = 0, \\ \dots \end{cases}$$


behavioral model

```


LIBRARY disciplines;
USE disciplines.electromagnetic_system.ALL;
LIBRARY ieee;
USE ieee.math_real.ALL;

ENTITY SORTBLOCK IS
GENERIC (
    \IB\ : REAL := 0.1E-3;
    \ISSQ1\ : REAL := 1.0E-16;
    \ISSQ2\ : REAL := 1.0E-16;

```

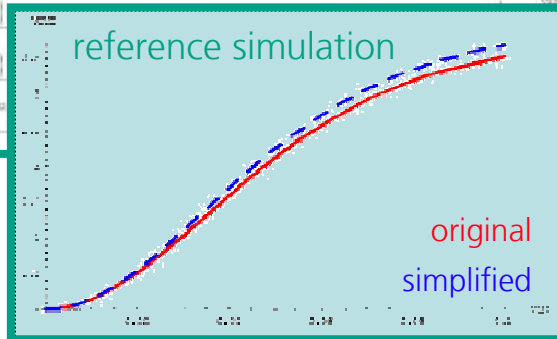

# Symbolic Model Reduction

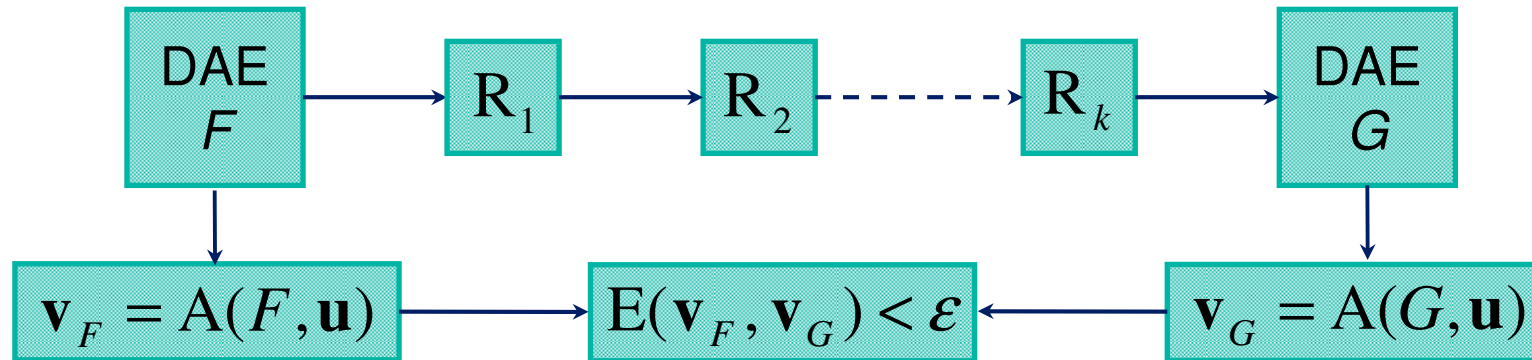

## ■ Specifications

- inputs  $u$ , outputs  $v$
- numerical analyses  $\mathbf{A}$

## ■ Error control

- error function  $\mathbf{E}$
- error bound  $\varepsilon$

## ■ Goal


- find DAE system  $G$  with reduced complexity and defined accuracy

## ■ Simplification process

- iterative application of reduction techniques  $\mathbf{R}$




# Symbolic Reduction Techniques (1)

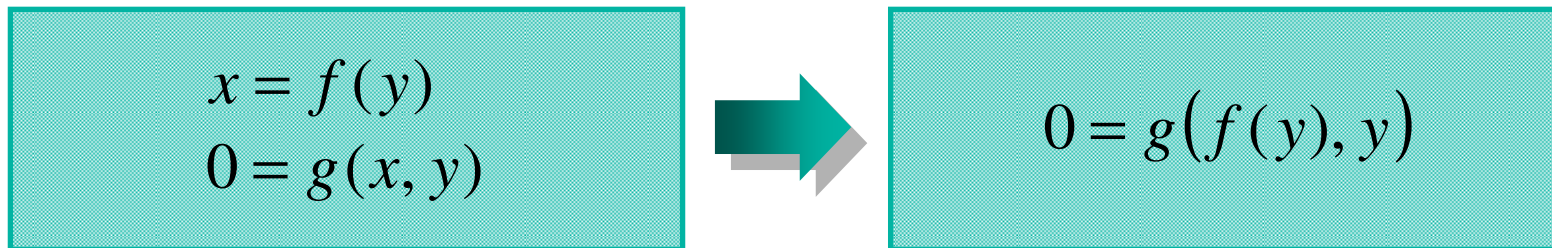

## ■ Algebraic manipulation

- elimination of variables
- removal of independent blocks of equations

$$\begin{aligned} & -I_{\$AC\$D1}[t] + C1 V_{\$2}'[t] == 0 \\ & -AREA_{\$D1} (-1 + e^{38.6635 (V_{\$1}[t] - V_{\$2}[t])}) IS_{\$D1} + I_{\$AC\$D1}[t] - GMIN (V_{\$1}[t] - V_{\$2}[t]) == 0 \end{aligned}$$

$$-AREA_{\$D1} (-1 + e^{38.6635 (V_{\$1}[t] - V_{\$2}[t])}) IS_{\$D1} + C1 V_{\$2}'[t] - GMIN (V_{\$1}[t] - V_{\$2}[t]) == 0$$

## Symbolic Reduction Techniques (2)

$$f(x) = \begin{cases} f_1(x) & x < a \\ f_2(x) & a \leq x \leq b \\ f_3(x) & x > b \end{cases} \quad \longrightarrow \quad f(x) = f_2(x) \quad \text{für alle } x$$

### ■ Branch reduction

- detection and removal of unused branches of piecewise-defined functions

idM3 ==

-If[-vdsM3 ≥ 0, If[1.11022 × 10<sup>-16</sup> - vgsM3 < 0, 0, If[1.11022 × 10<sup>-16</sup> - vgsM3 ≤ -vdsM3,  $\frac{0.5 \text{ KP}M3 (1.11022 \times 10^{-16} - \text{vgs}M3)^2 \text{ W}M3}{L\text{M3}}$ ,


$$\left. \begin{aligned} & - \frac{1. \text{ KP}M3 \text{ vds}M3 (1.11022 \times 10^{-16} + 0.5 \text{ vds}M3 - \text{vgs}M3) \text{ W}M3}{L\text{M3}} \right], \\ & \text{If}[1.11022 \times 10^{-16} - \text{vgs}M3 < 0, 0, \text{If}[1.11022 \times 10^{-16} - \text{vgs}M3 \leq \text{vds}M3, - \frac{0.5 \text{ KP}M3 (1.11022 \times 10^{-16} - \text{vgs}M3)^2 \text{ W}M3}{L\text{M3}}, \\ & \left. \left. \left. \frac{. \text{ KP}M3 \text{ vds}M3 (1.11022 \times 10^{-16} - 0.5 \text{ vds}M3 - \text{vgs}M3) \text{ W}M3}{L\text{M3}} \right] \right] \right] \end{aligned} \right\}$$

idM3 == -If[-vdsM3 ≥ 0,  $\frac{0.5 \text{ KP}M3 (1.11022 \times 10^{-16} - \text{vgs}M3)^2 \text{ W}M3}{L\text{M3}}$ , 0]



## Symbolic Reduction Techniques (3)

$$F_j : \sum_{i=1}^N t_i(x) = 0$$

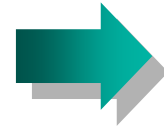

$$G_j : \sum_{\substack{i=1 \\ i \neq k}}^N t_i(\tilde{x}) + \kappa = 0$$

### ■ Term substitution

- replace terms of equations with constant value
- applicable to nested expressions

$$\text{-AREA\$D1} (-1 + e^{38.6635 (V\$1[t] - V\$2[t])}) \text{IS\$D1} + \text{I\$AC\$D1} [t] - \text{GMIN} (V\$1[t] - V\$2[t]) == 0$$




$$\text{-AREA\$D1} (-1 + e^{38.6635 (V\$1[t] - V\$2[t])}) \text{IS\$D1} + \text{I\$AC\$D1} [t] - \text{GMIN} (12. - V\$2[t]) == 0$$



## Symbolic Reduction Techniques (4)

$$F_j : \sum_{i=1}^N t_i(x) = 0$$

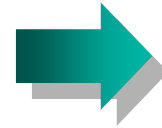

$$G_j : \sum_{\substack{i=1 \\ i \neq k}}^N t_i(\tilde{x}) = 0$$

### ■ Term reduction

- replace terms of equations with zero
- applicable to nested expressions

$$\text{-AREA\$D1 (-1 + e}^{38.6635 (V\$1[t]-V\$2[t])} \text{) IS\$D1 + IS\$AC\$D1 [ t] - GMIN (V\$1 [ t] - V\$2 [ t] ) == 0}$$



$$\text{-AREA\$D1 (-1 + e}^{38.6635 (V\$1[t]-V\$2[t])} \text{) IS\$D1 + IS\$AC\$D1 [ t] == 0}$$



---

# Overview

Motivation for symbolic methods

Symbolic techniques



Hierarchic systems

Workflow for exploitation of the hierarchy

# New Challenges

- growing miniaturization of integrated circuits  
→ nanoelectrical structures
- increasing integration density of circuit components  
→ non-negligible physical effects


↗ Model descriptions based on **PDEs!**

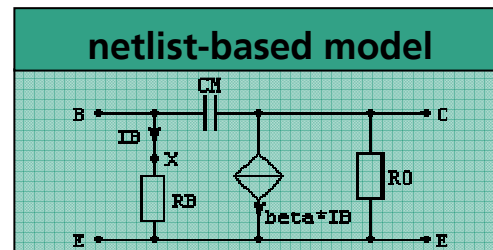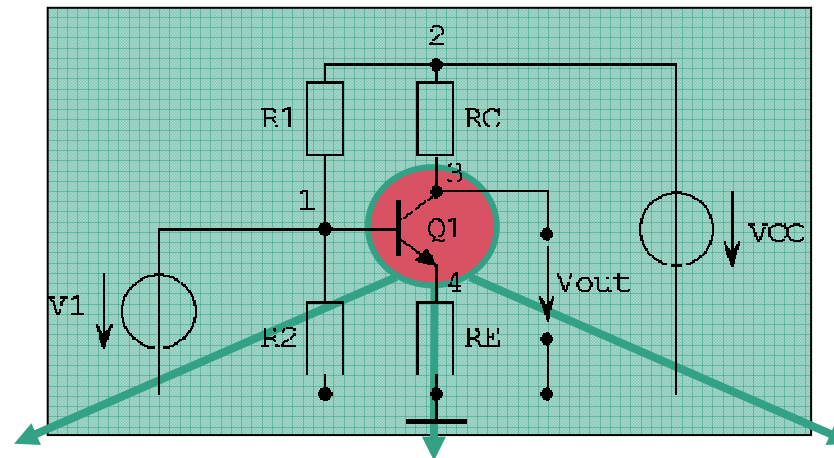

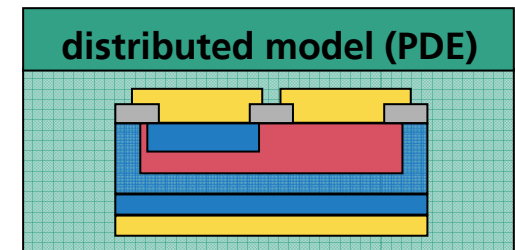**behavioral model (DAE)**

```

b$Vbc = "VBC$ac" - b$IB*IB$ac + b$RC
b$Vbe = "VBE$ac" - b$rb*IB$ac - b$RE
b$Vbx = "VBC$ac" + b$RC*Temp/"AREA"*IC
b$Kqb = 0.5*(1.+LimPower[1.+4.*(
("AREA"*b$ISTemp*(Exp[b$Sign*b$V
+ b$Sign*b$Vbe*"GMIN") / ("ARE
+ ("AREA"*b$ISTemp*(Exp[b$Sign*
+ b$Sign*b$Vbc*"GMIN") / ("A
) "NK"1
    
```





Fraunhofer Institut  
Techno- und  
Wirtschaftsmathematik


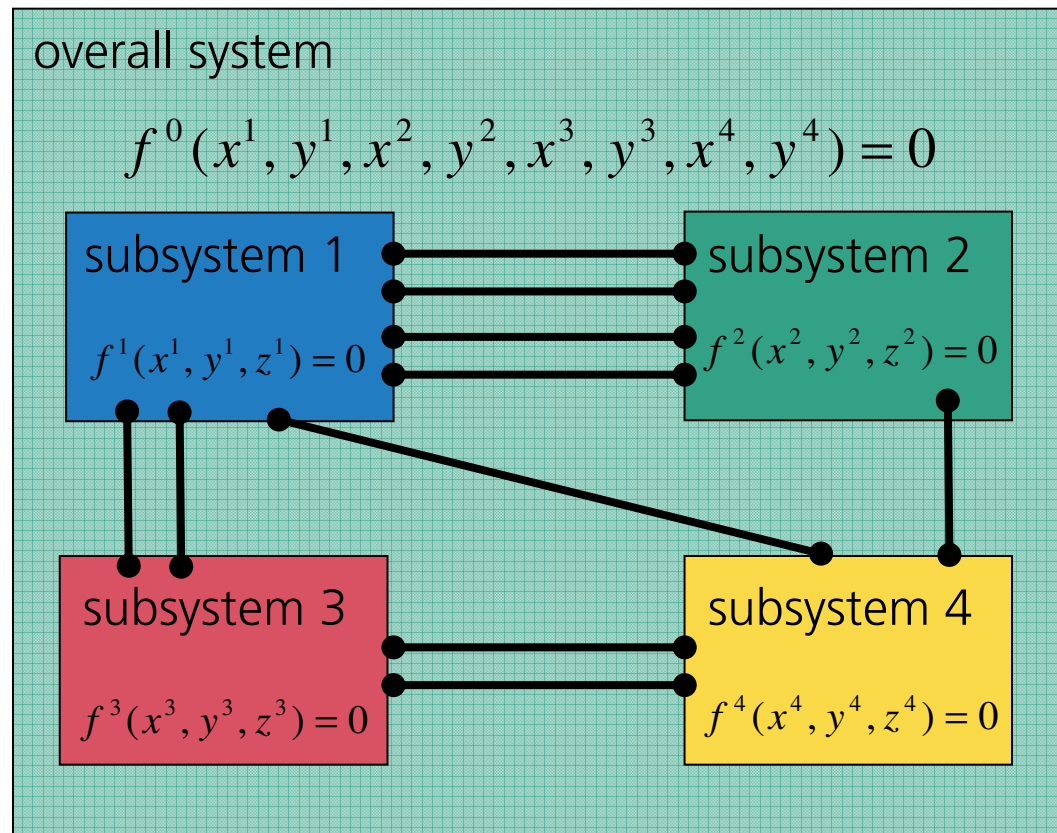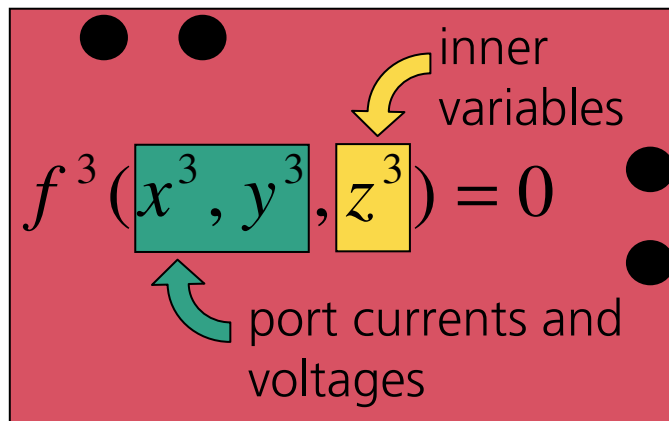
# Hierarchic Modelling


→ various components / subsystems using *different mathematical descriptions*, coupled by a topology

**currently:** "flat" hierarchy  
**goal:** *structure exploitation*



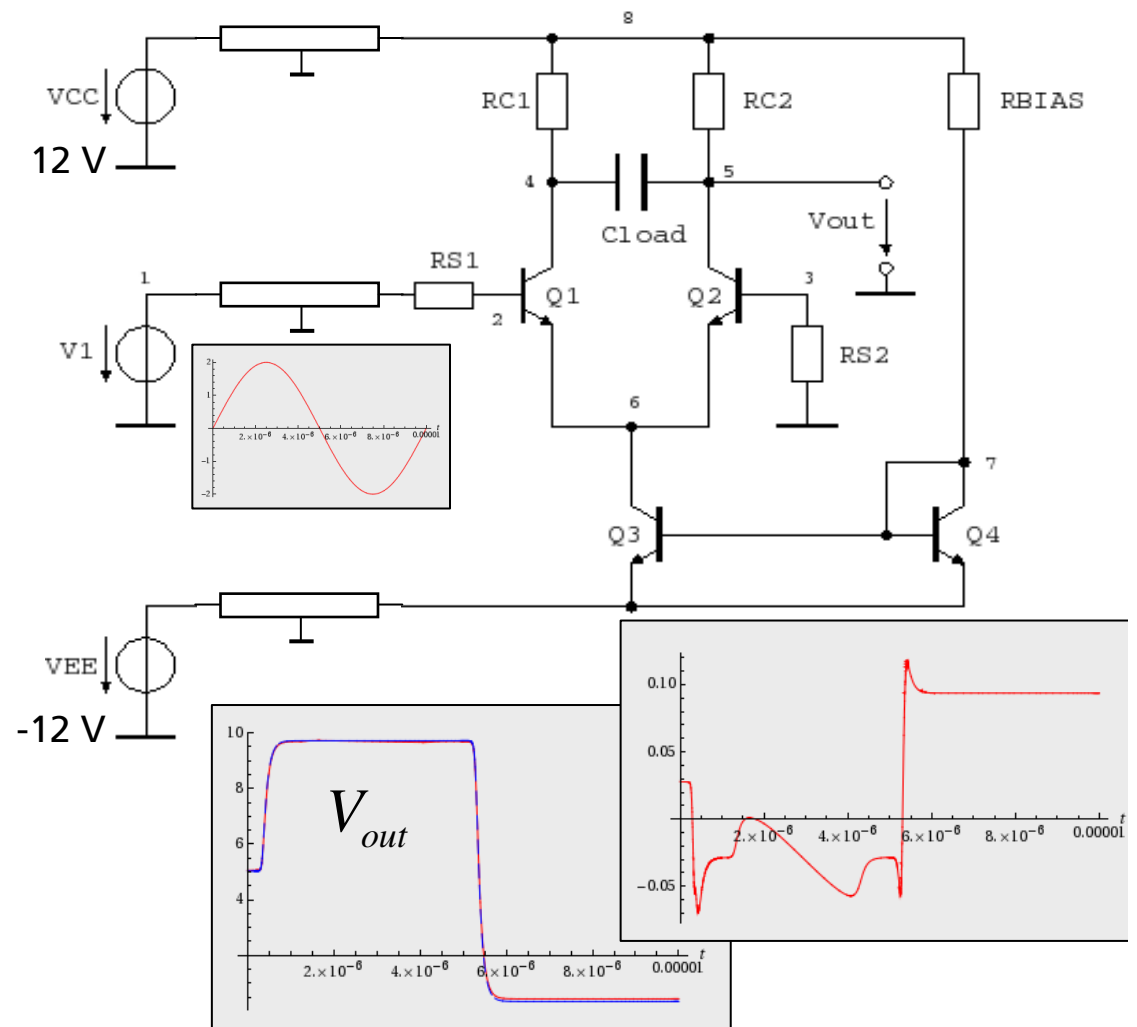
# Differential Amplifier Circuit

- “long distance” transmission lines between sources and components
- discretized PDE model with 20 line segments
- full system:  
167 equations, 645 terms
- symbolic reduction:  
124 equations, 425 terms,  
2% error in magnitude permitted,  
approx. 2 hours and 10 minutes



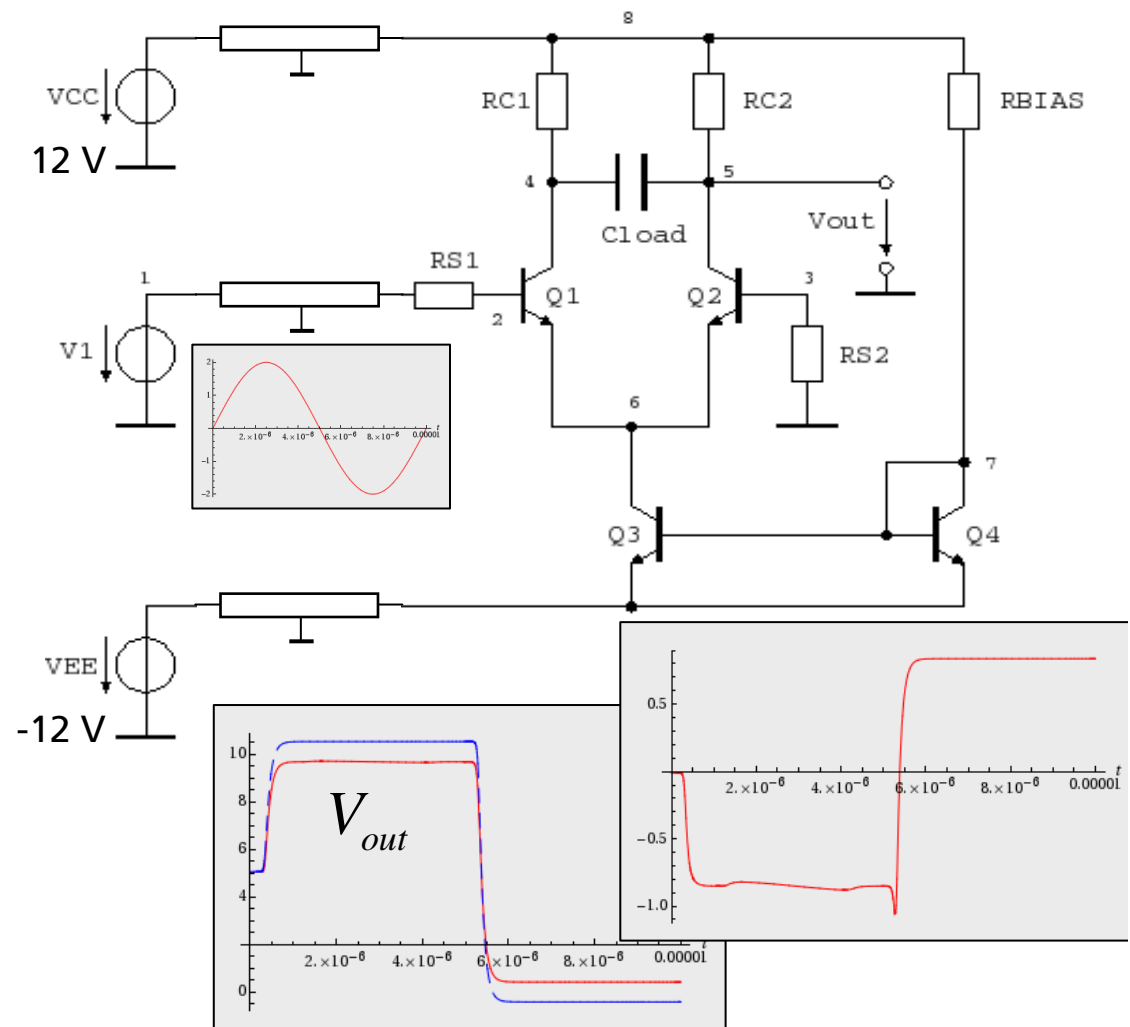
# Differential Amplifier Circuit

- “long distance” transmission lines between sources and components
- discretized PDE model with 20 line segments
- full system:  
167 equations, 645 terms
- symbolic reduction:  
44 equations, 284 terms,  
10% error in magnitude permitted,  
approx. 2 hours and 10 minutes


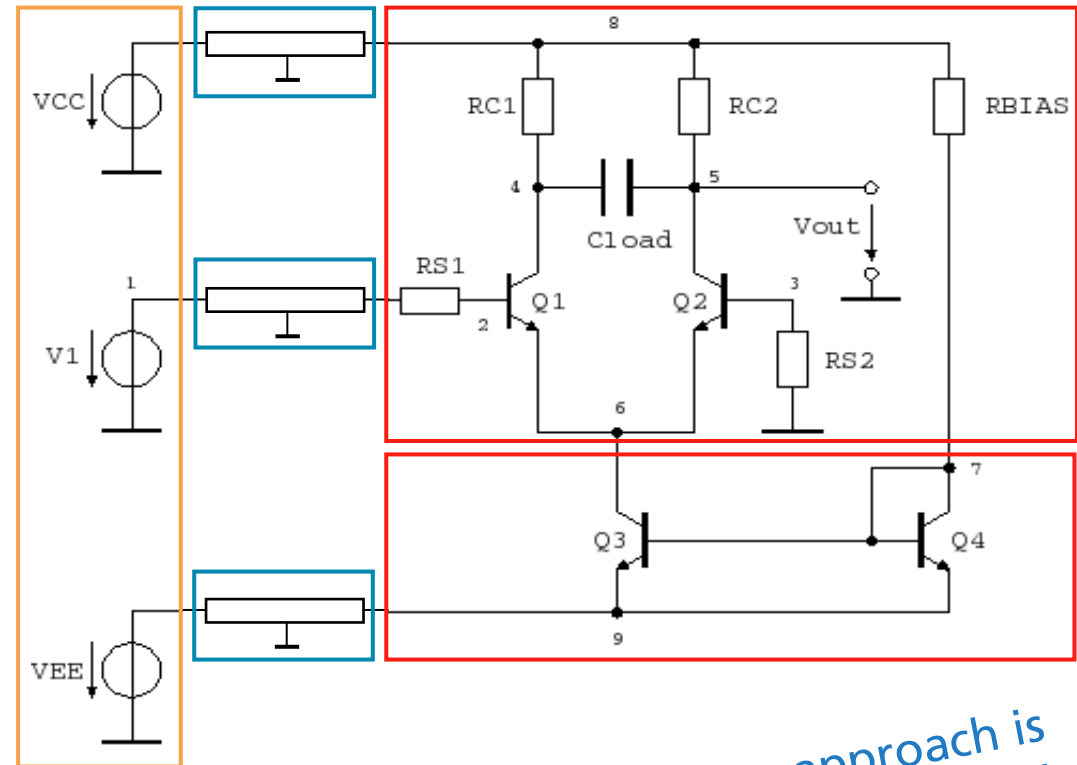
# Differential Amplifier Circuit

- “intuitive” hierarchy
- standard graph theoretical methods like MNA / STA lose this information



A modelling approach is aspired that transmits this information into the set of equations!

$$I_{CS}^{Q3} + I_{ES}^{Q1} + I_{ES}^{Q2} = 0$$


$$I_{R0}^{Rleitung1} + \frac{-V_{2} + V_{X1}}{R_{S1}} = 0$$

$$I_{ES}^{Q3} + I_{ES}^{Q4} + I_{R0}^{Rleitung9} = 0$$


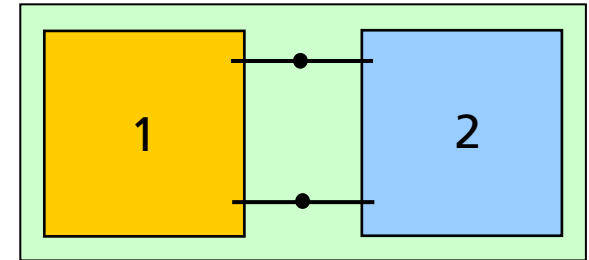
# Macro Modelling


Goal:  $f_1(u_1, i_1, x_1) = 0$   
 $f_2(u_2, i_2, x_2) = 0$



Idea:

use port currents and voltages  
instead of branch magnitudes!

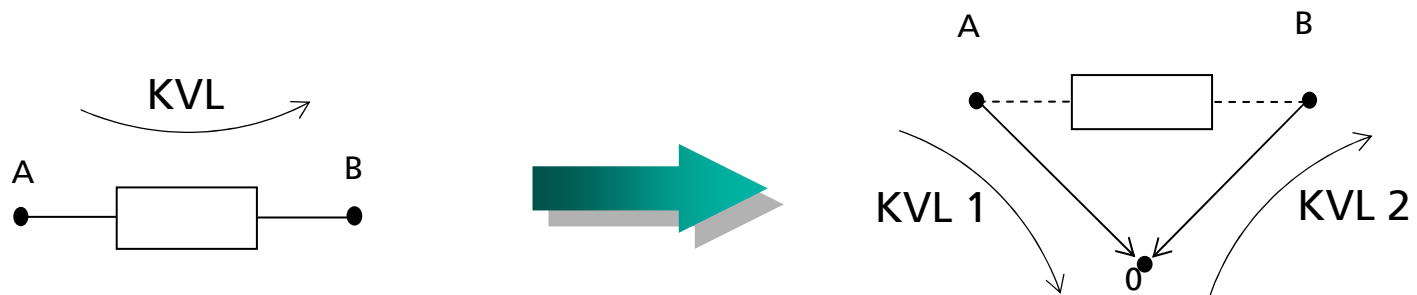Side effect:  $u_1 = u_2$   
 $i_1 + i_2 = 0$



---

# Overview

Motivation for symbolic methods







Symbolic techniques

Hierarchical systems




Workflow for exploitation of the hierarchy

---

# Workflow

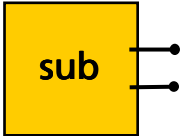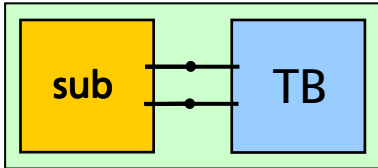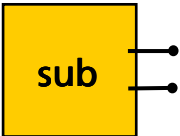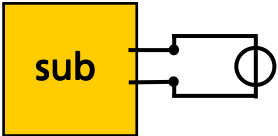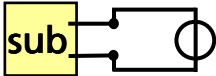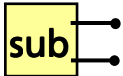- plug  in a testbench: 
- record voltages at the ports
- plug a voltage source to  that delivers exactly the recorded voltages as PWL function
- reduce the circuit  with appropriate symbolic or numerical methods
- finally remove the voltage source from the reduced circuit  and receive a reduced subsystem 

# Differential Amplifier Circuit

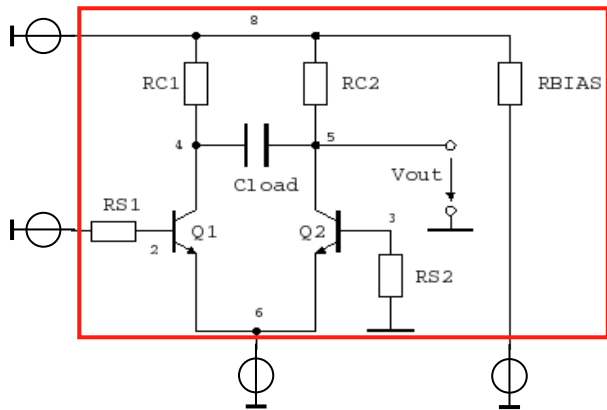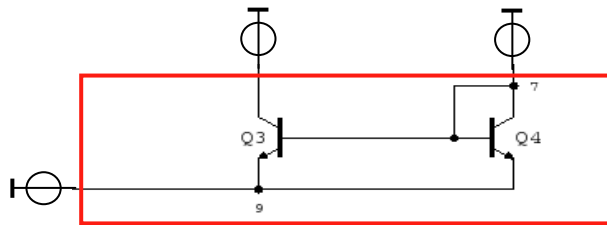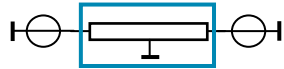

- numerical reduction via state space form and Arnoldi's algorithm within seconds:  
50  $\Rightarrow$  8 resp. 4 equations
- symbolic reduction within seconds (2% error permitted):  
16  $\Rightarrow$  9 equations,  
59  $\Rightarrow$  20 terms
- symbolic reduction within seconds (2% error permitted):  
22  $\Rightarrow$  13 equations,  
91  $\Rightarrow$  50 terms

*Almost no changes if 10% error is permitted!*







# Differential Amplifier Circuit

- plug together all the reduced subsystems:  
167  $\Rightarrow$  62 equations,  
645  $\Rightarrow$  252 terms

Mostly dependent on the numerical reduction of the conductors!

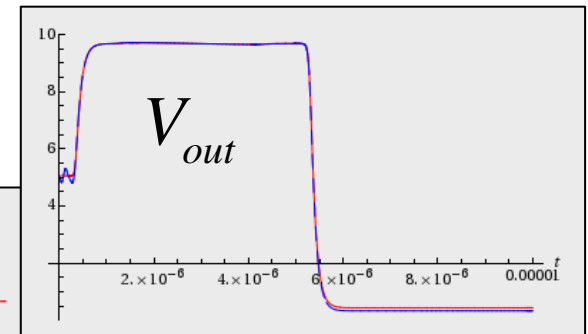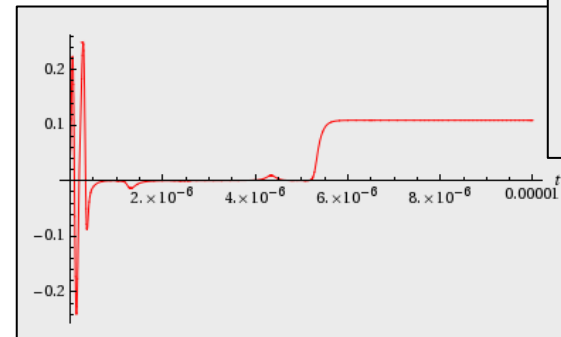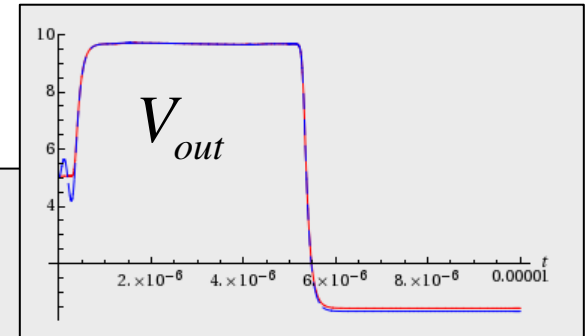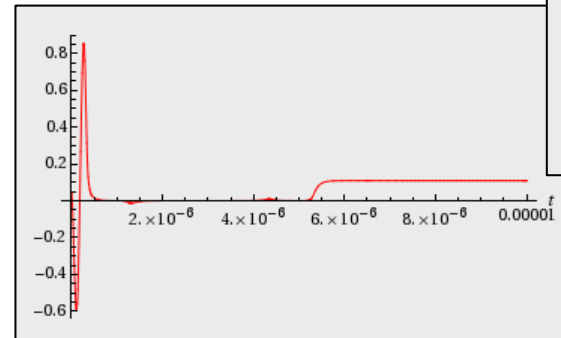- by using more modes of conductor1 (12 equations):  
167  $\Rightarrow$  66 equations,  
645  $\Rightarrow$  396 terms



---

# Summary and Outlook

- Proof of concept: Workflow delivers good results for the small circuit example
  - coupling of different subsystems with different mathematical descriptions
  - application of dedicated MOR techniques
- How to get and what is a good segmentation of the overall circuit into subsystems?
- Automatic detection of hierarchical structure.
- Reduce subsystems  $1, \dots, k \Rightarrow \mathcal{E}_1, \dots, \mathcal{E}_k$ . What about  $\mathcal{E}_{ges}$  ?

---

Thank you for your attention.