
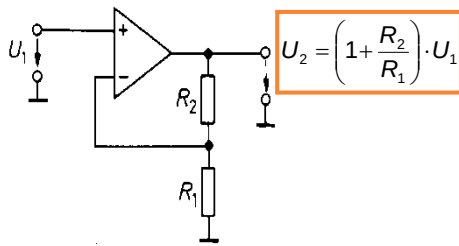


Overview of Op-Amp Circuits


Constant voltage source

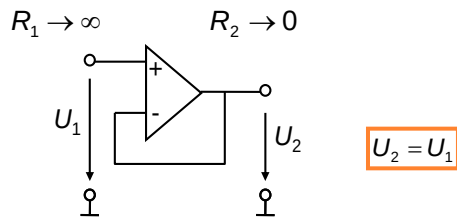


Voltage follower / Impedance transformer




Inverter

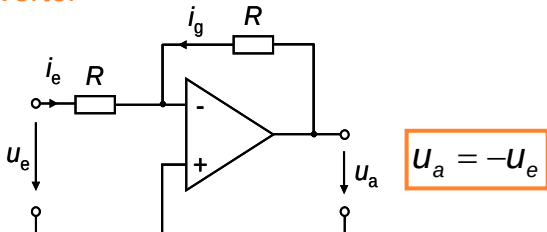


Summer

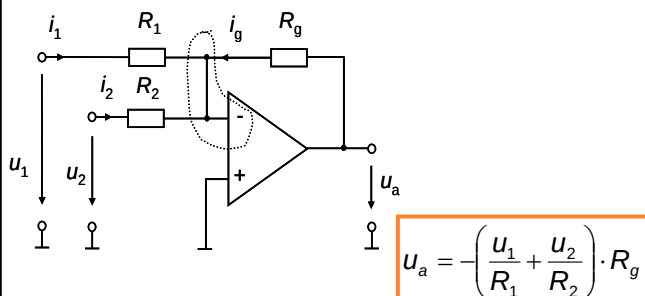


Subtractor

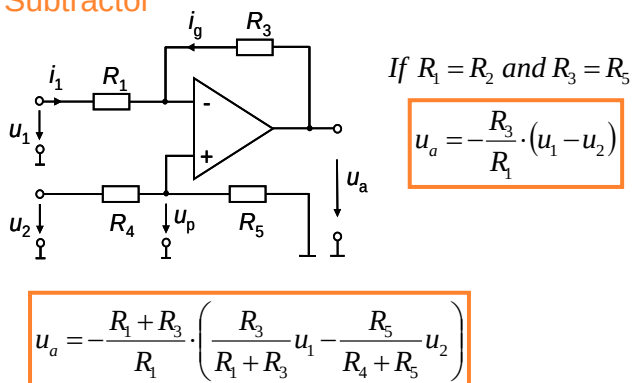


Schmitt-Trigger (clock generator)

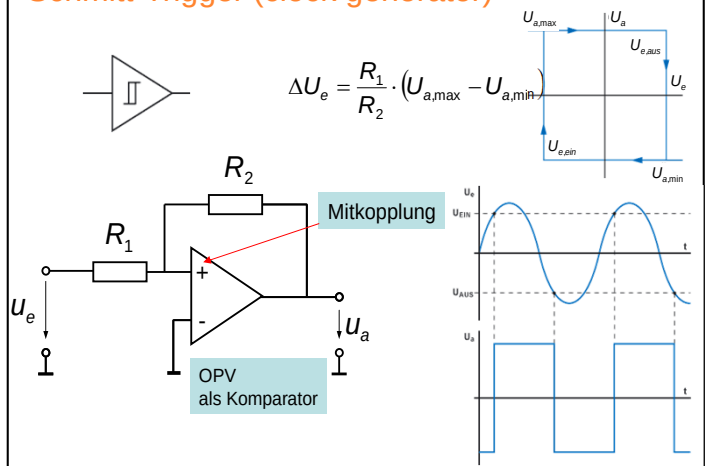

Differentiator

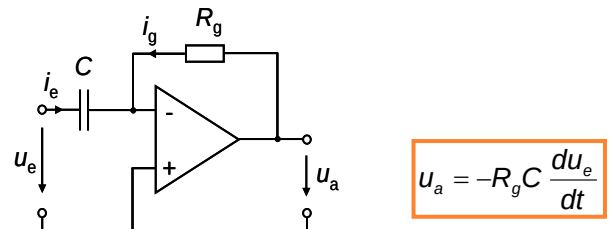

Integrator

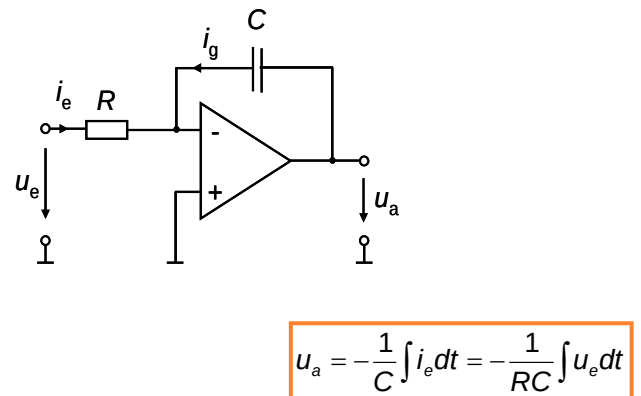

Logarithm

