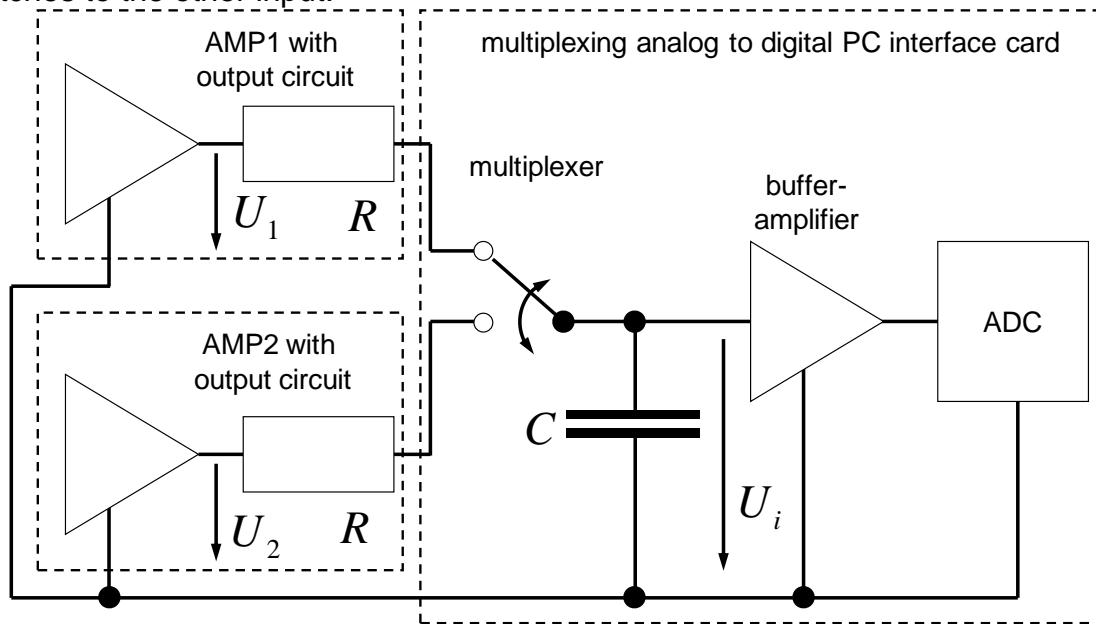


## multiplexing analog to digital converter PC interface card

The signal of two sensors should be measured using a multiplexing analog to digital converter PC interface card. Sensor signals are amplified with operational amplifiers. The output signals of the amplifiers are directly connected to the input of the PC-interface card. The PC interface card consists of one analog to digital converter (ADC) and one multiplexer. After each conversion of an analog value the multiplexer switches to the other input.



technical data of the PC interface card

- ADC conversion rate 100kS/s
- ADC resolution 16 bit
- Input capacitance  $C=100\text{pF}$


The output signals of the operational amplifiers are  $-1\text{V} < U < 1\text{V}$ .

- Calculate the absolute value of the quantization error. The whole output range of the operational amplifier is quantized with the resolution of the ADC.
- How long are the times, while the output signals of the AMP1 and AMP2 are connected to the buffer amplifier? Use a drawing to give a reason for your decision.
- Errors because of aliasing must be avoided. How big is the value of the maximum allowed frequency contained in the signals  $U_1$  and  $U_2$ ?
- The multiplexer switches from output voltage of AMP1 to the output voltage of AMP2. Calculate the timely behavior of voltage  $U_i$  after the multiplexer switched from voltage  $U_1$  to voltage  $U_2$ . Plot the behavior of voltage  $U_i$  into a diagram.
- The maximum error because of recharging the input capacitor  $C$  should be less than the absolute quantization error. What is the maximum allowed value of the operational amplifiers output resistor  $R$ ?
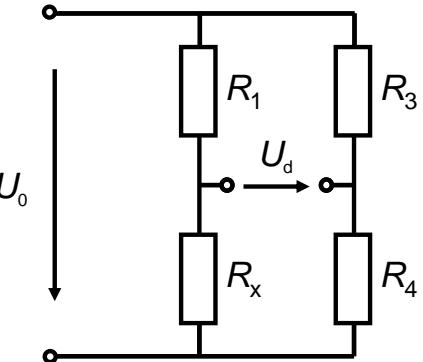
## bridge circuit in unbalanced mode


The figure shows a bridge circuit in unbalanced mode for measuring a resistance change of  $R_x$ .

- How  $R_1$ ,  $R_3$ ,  $R_4$  must be selected for balancing the bridge to  $U_D = 0 V$  when  $R_{x0} = 1 k\Omega$ . The sensitivity  $dU_D/dR_x$  should have its maximum at  $R_{x0}$ ?
- The maximum power at  $R_x$  should be  $P_{W\max} = 0,125 W$ . What must be the value of  $U_E$  when  $R_{x0} = 1 k\Omega$ ?
- For small resistance changes of  $R_x$  ( $\Delta R_x \ll R_{x0}$ ) the bridge voltage can be approximated by  $U_d \approx -U_0 \cdot \frac{\Delta R_x}{4R_{x0}}$ . The error because of the approximation should be smaller than 1%. What is the allowed maximum value of  $\Delta R_x$ ?


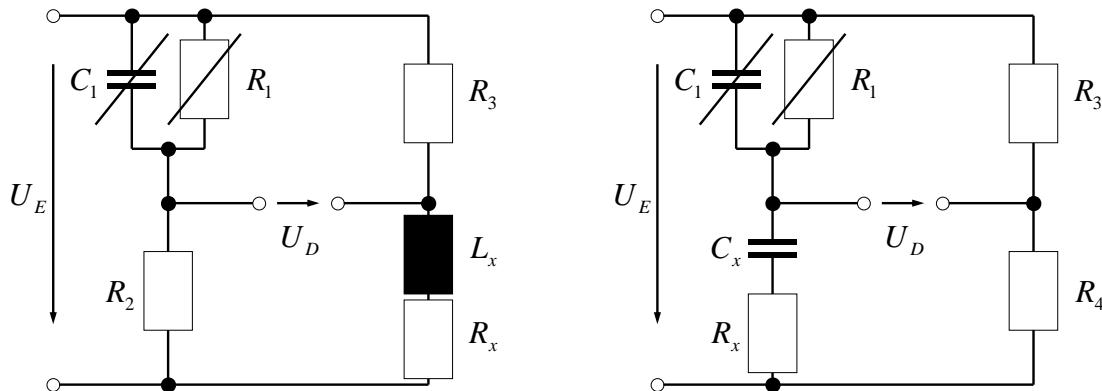
## balancing AC bridges

The following bridge circuits are used for measuring capacitances and inductances and their losses.



- Calculate the impedances  $Z_1$ ,  $Z_2$ ,  $Z_4$  und  $Z_4$  and the conditions for balancing the bridges.
- The values of  $R_1$  and  $C_1$  are used to balance the bridges. Calculate the values of unknown quantities  $R_x$  and  $L_x$  and  $R_x$  and  $C_x$  depending on the values of  $R_1$  and  $C_1$  in balanced condition.
- Draw a bridge that cannot be balanced. Give a reason for your decision.