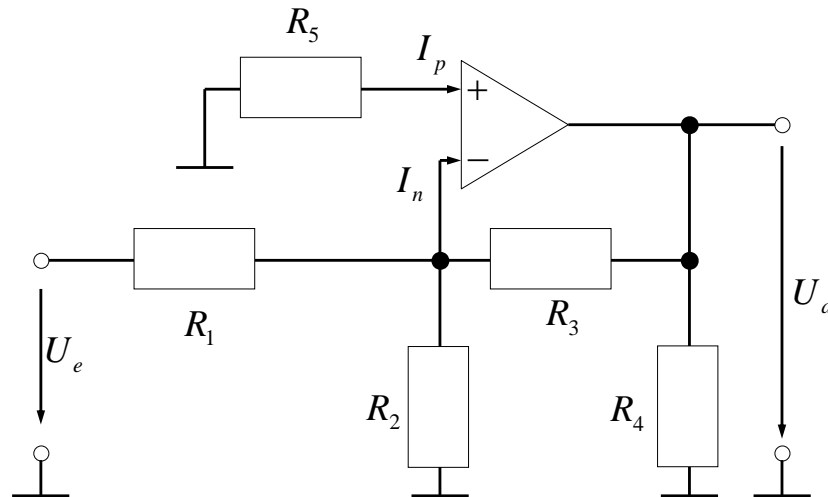


## non ideal operational amplifier


Within this exercise the input bias currents  $I_p$  and  $I_n$  of a real operational amplifier will be considered.



- Is the operational amplifier working as inverting or non-inverting amplifier?
- Give an estimate value for the input bias currents  $I_n$  and  $I_p$  of a real operational amplifier. What is the order of magnitude for a real operational amplifier?
- How the bias currents  $I_n$  and  $I_p$  can be considered by using the model of an ideal operational amplifier? Redraw the given circuit using the model of the ideal operational amplifier by also considering the input bias currents.
- Calculate the voltage  $U_a$  depending on  $U_e$  with also considering the bias currents  $I_n$  and  $I_p$ .
- What is the meaning of  $R_5$ ?
- The input bias currents should be compensated. Calculate the value of  $R_5$  so that input bias currents do not cause an influence on the output voltage  $U_a$ .
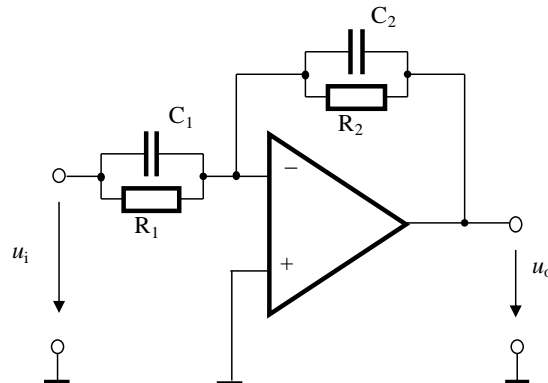
## general analog filters


A method for realizing filters, an integrator and a differentiator will be considered.



- Calculate the transfer function of the circuit. The operational amplifier is assumed to be ideal.
- Under which conditions the circuit will become
  - An integrator
  - A differentiator?
- Plot the bode diagram of an ideal integrator and an ideal differentiator.
- What happens when replacing capacitor  $C_2$  by an inductor  $L$ ?
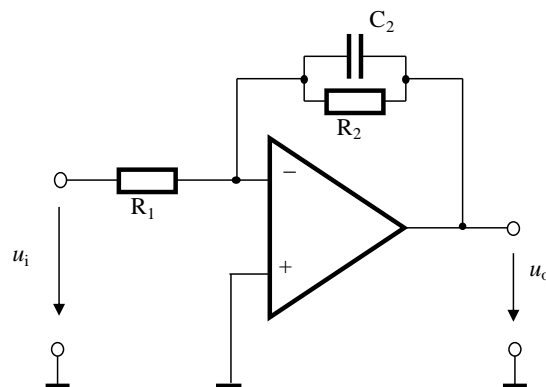
## design of simple filter circuit

A certain transfer function should be realized with this operational amplifier circuit. The value of the resistor  $R_2$  is  $100\text{k}\Omega$ .



- Calculate the values of the remaining unknown elements. These conditions must be fulfilled:
  - At a frequency of  $0\text{Hz}$  the absolute value of the amplification is 100.
  - At a frequency of  $1\text{MHz}$  the absolute value of the amplification is 1.
- At which frequency the value of the amplification is 50?