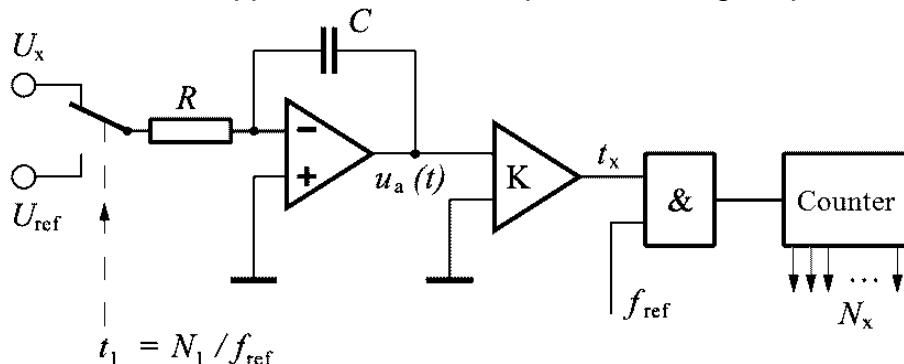



Dual Slope ADC

The dual slope analog-digital-converter according to the figure is an integrating converter. The unknown voltage U_x is integrated up during known measurement time t_1 . Subsequently the reference voltage U_{ref} is integrated down to zero. The measurement time t_x is proportional to the unknown voltage U_x . Integrating converters are useful to suppress inductive coupled disturbing frequencies



- During down integration time t_x pulses with the frequency f_{ref} at the output of the AND-gate are counted. What is the relationship between the counter N_x and the factor N_1 , the unknown voltage U_x ($U_x = \text{constant!}$) and the reference voltage U_{ref} ?
- An unknown voltage of $U_x = -1/3 U_{ref}$ should be measured with an accuracy of 0,1 %. What must be the corresponding value of the factor N_1 ?
- How long is the minimum measurement time $t_{1,\min}$ to suppress disturbing frequencies of 50Hz, 60Hz and 50Hz and 60Hz simultaneously?
- An unknown voltage of $U_x = -1/3 U_{ref}$ should be measured with an accuracy of 0,1% and disturbing frequencies of 50Hz and 60Hz should be suppressed. What is the corresponding value of the reference frequency f_{ref} ?
- The values of R , C and f_{ref} are changing because of aging of the components. What is the influence on the counter N_x ?

Incremental Follow-Up-Converter

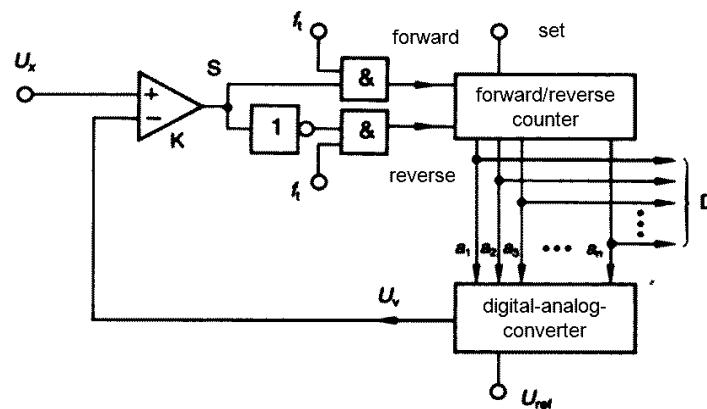


The Incremental Follow-Up-Converter: has the following technical data:

- Input voltage range $U_x = (0V \dots 5V)$
- resolution $\leq 20 \text{ mV}$
 - What is the bit-resolution of the digital analog converter?
 - A sinusoidal input voltage with 5V amplitude and 10kHz frequency should be converted without any delay. What is the allowed minimum clock rate?

- c) The digital analog converter has a delay time of 10ns. The comparator has a delay time of 250ns. What is the effect on the output digital word? The input voltage is a constant DC voltage.
- d) The converter should work without any disturbing effects. This is fulfilled while $|U_x - U_v| \leq U_{LSB}$. What is the maximum allowed delay time of the comparator? The input voltage is a constant DC voltage.

Digital-Analog-Converter

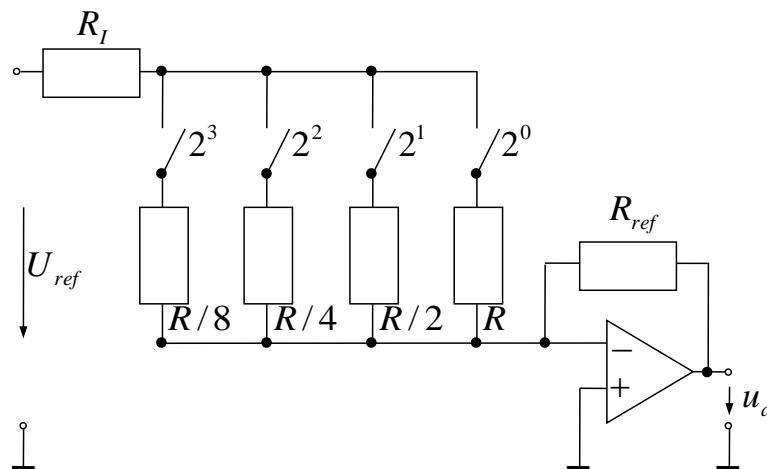

- a) Calculate the value of the reference resistor R_{ref} . The following values are known: $R_I = 0\Omega$, $R = 100\text{k}\Omega$, $U_{ref} = 1,2 \text{ V}$. The digital word is $Z = 1111$ what means that all switches are closed and the corresponding output voltage is $u_{A,\min} = -5 \text{ V}$.
- b) The inner resistor R_I of the voltage source U_{ref} causes an error. Which digital word Z causes the biggest error on the output voltage u_A ?
- c) The inner resistor R_I of the voltage source U_{ref} has an value of $R_I = 100 \Omega$. Calculate the value of the error on the output voltage u_A . Use the values of a).
- d) The error on the output voltage should be constant at all digital words D . How the resistor network must be changed?