

5 Analog Signal Processing- Data Acquisition

5.1 Analog Measurement Procedures

5.2 Measurement of Resistances

Three- and Four-Wire-Method, Self-Heating
¼-Bridge, ½-Bridge, and Full-Bridge

5.3 Measurement of Capacitances and Inductivities

5.3.1 AC-Current-Bridges

Adjustability

Frequency dependent Adjustability

5.3.2 Measurement with Oszillator

5.3.3 Charge-Transfer Method for Measurement of Capacitances

5.3.4 Power Measurement Method

5.4 Computer-based Data Acquisition

5.1 Analog Measurement Procedures

Why analog measurement procedures?

Most sensors have an analog output signal

Current, voltage, resistance

Low-cost signal processing and realization

No quantization-error and no conversion time




Analog measurement systems can be faster!


5.1 Analog Measurement Procedures

Impedance

ideal

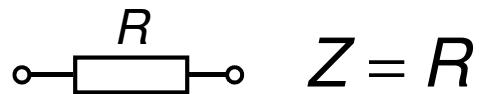

$$\underline{Z} = R$$

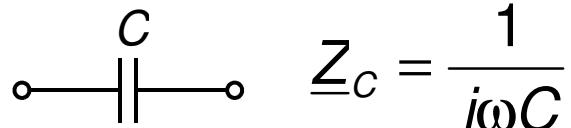


$$\underline{Z}_C = \frac{1}{j\omega C}$$




$$\underline{Z}_L = j\omega L$$

real

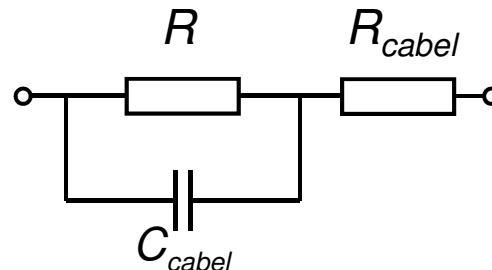
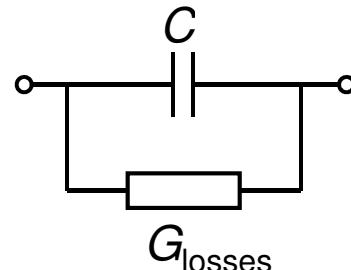
$$\underline{Z} = R_{cable} + R \parallel j\omega C_{cable}$$



$$\begin{aligned}\underline{Y}_{real} &= G_{losses} + jB \\ &= G_{losses} + j\omega C\end{aligned}$$

$$\underline{\epsilon}_r = \epsilon'_r - j\epsilon''_r$$

$$= \frac{B}{\omega C_0} - j \frac{G}{\omega C_0}$$




$$\underline{Z}_{L,real} = R_{Coil} + j\omega L$$

5.2 Measurement of Resistances

4-Wires-Method


2-Wires-Method

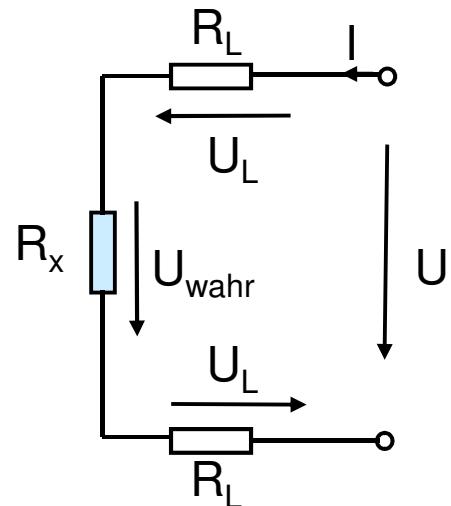

Error by

- Temperature dependence of wires
 \neq Cable length $\rightarrow \neq R_L$

4-Wires-Method

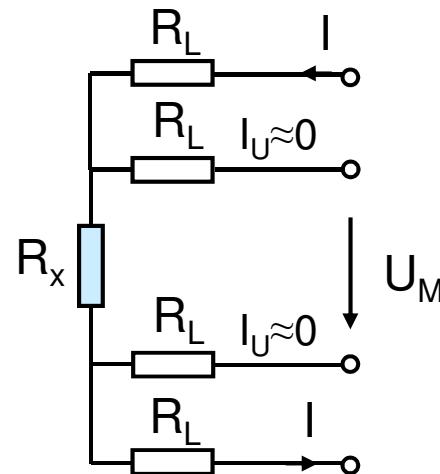


$$R_x = \frac{U_M}{I}$$

Total separation between current- and voltage-wires

5.2 Measurement of Resistances

3-Wires-Method


2-Wires-Method

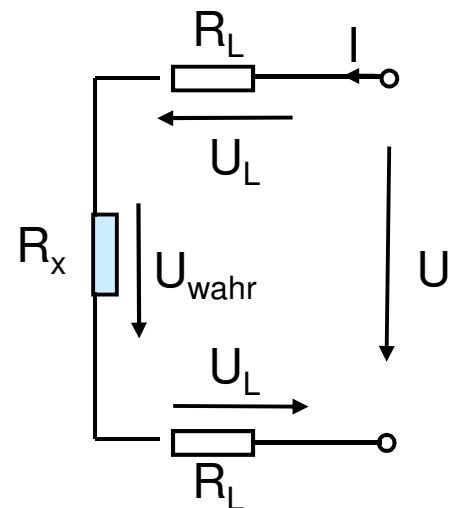

Error by

- Temperature dependence of wires
 \neq Cable length $\rightarrow \neq R_L$

3-Wires-Method

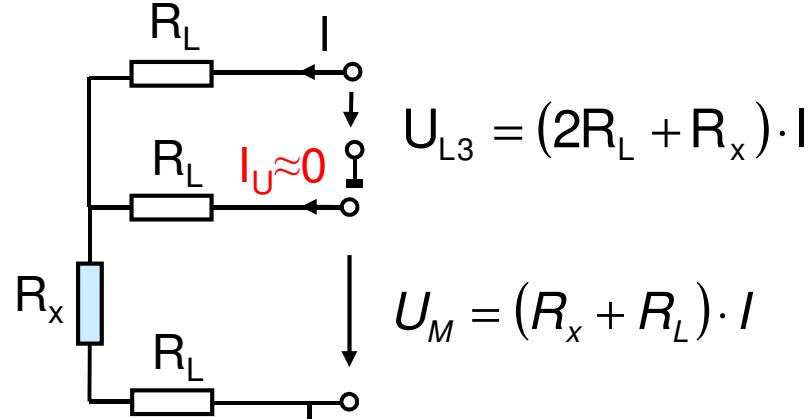

$$U_{L3} = 2U_M - R_x I$$

$$R_L = \frac{U_M}{I} - R_x$$

$$R_x = \frac{2U_M - U_{L3}}{I}$$


→ Compensation of cable resistance and its temperature dependence

Prerequisite

- 3 wires have the identical length and temperature

5.2 Measurement of Resistances

Self-Heating

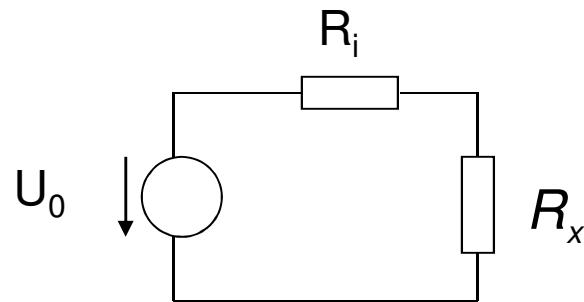

Converted electric power

$$P = I^2 R_x = \left(\frac{U_0}{R_i + R_x} \right)^2 \cdot R_x$$


Self-heating through accumulated heat ΔT_{th}

$$\Delta T_{th} = R_w \cdot P$$

R_w : Heat resistance is dependent on:

- Packaging
- Surrounding media, its temperature and velocity!
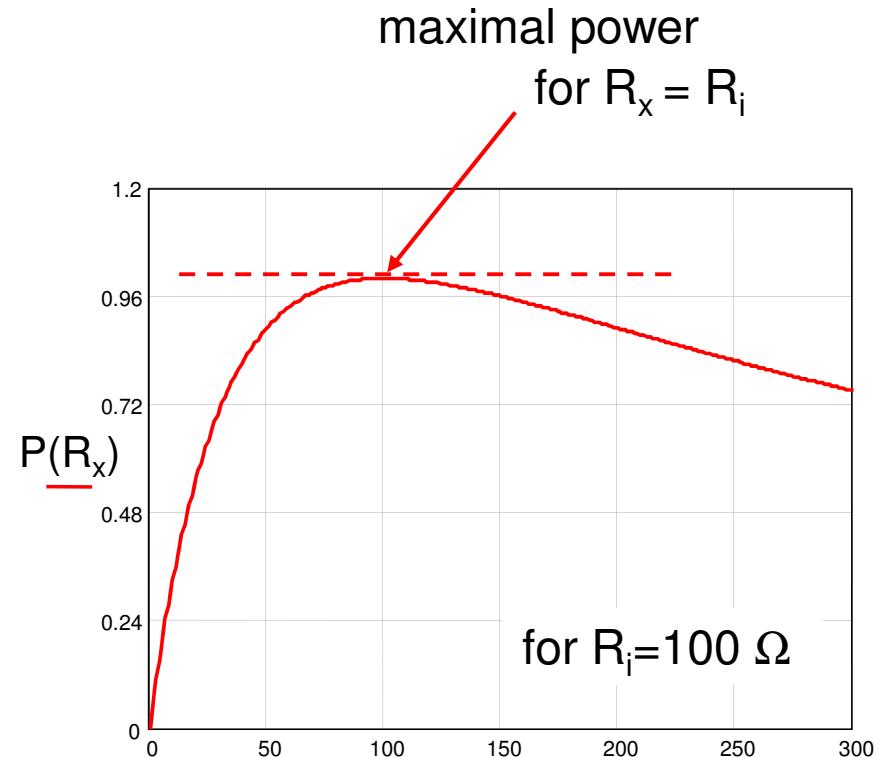
$$\frac{\partial P}{\partial R_x} = \left(\frac{U_0}{R_i + R_x} \right)^2 \cdot \frac{R_i - R_x}{R_i + R_x}$$



5.2 Measurement of Resistances


Comparison with a reference resistance (reference principle)

$$R_x = \frac{U_x}{U_r} R_r$$

R_r and R_x should have the same order of magnitude

→ Reduction of uncertainty through common mode rejection

Typical values $R_r = R_{x, \text{max}}$

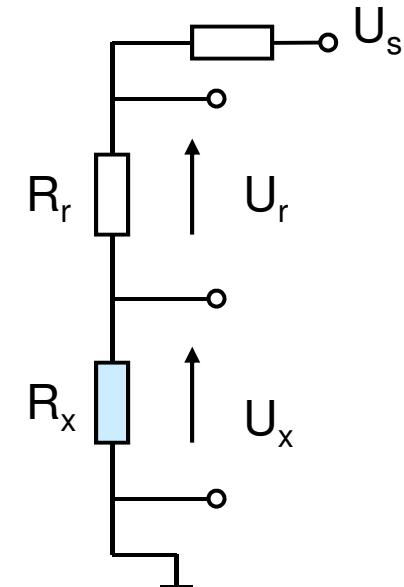

R_r : Reference resistance

R_x : Resistance to be measured

5.2 Measurement of Resistances

Voltage Divider

Suitable for high resistance values

$$U_0 = \frac{R_r}{R_r + R_x} \cdot U_r$$

$$R_x = R_r \frac{U_0}{U_r - U_0}$$



Nonlinear, because the current is unknown

Example:

$$R_r = k R_0$$


$$R_x = R_0(1 + x)$$
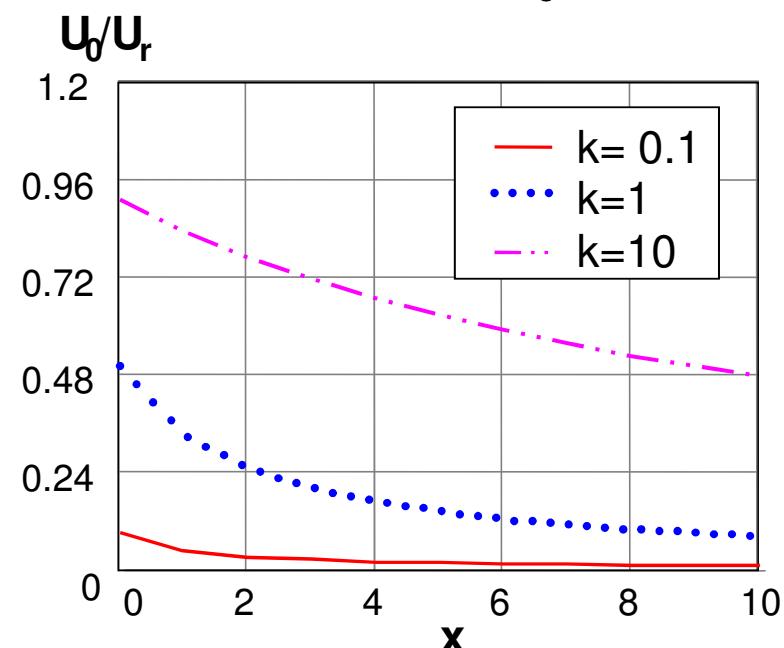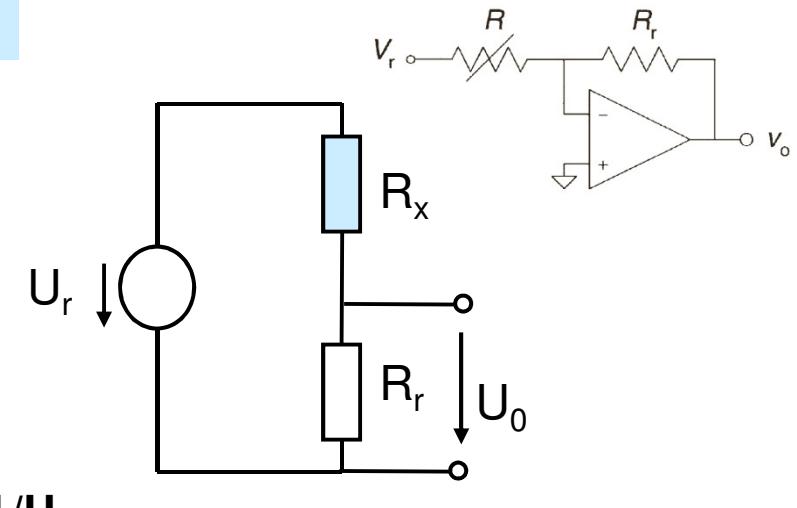
$$\frac{U_0}{U_r} = \frac{k}{k + 1 + x}$$




5.2 Measurement of Resistances

Inverting Amplifier

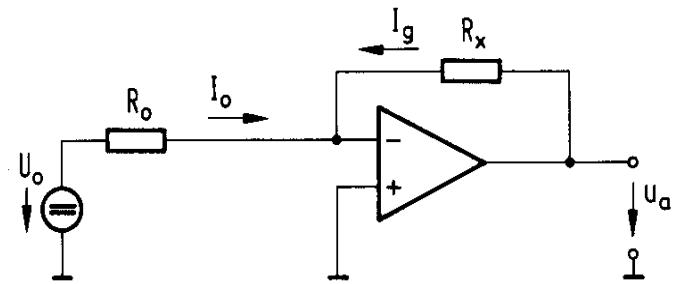


Supply with a constant voltage

$$U_a = -\frac{U_o}{R_o} R_x$$

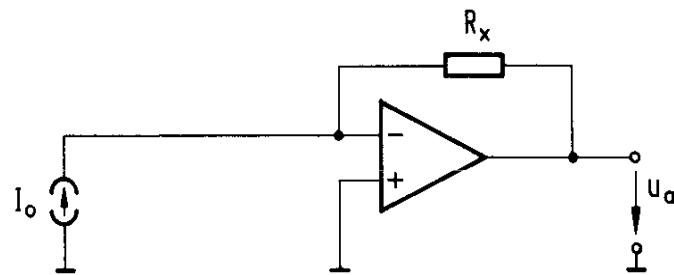

Supply with a constant current

$$U_a = -I_o R_x$$

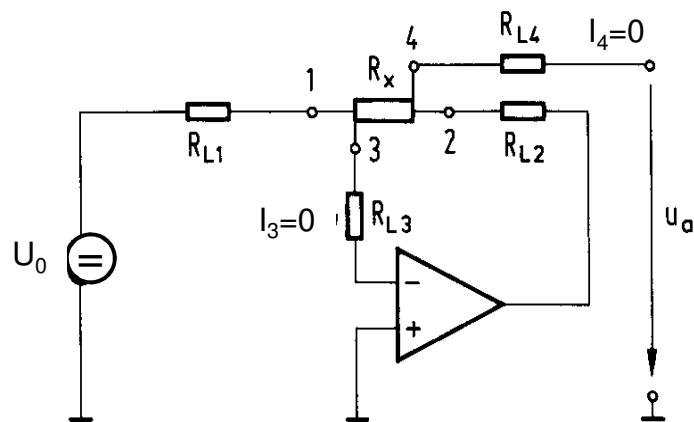

4-Wires-connection and constant current supply

$$U_a = -I_0 R_x$$

Offset-currents and offset-voltages are problematic if resistances have small changes!

5.2 Measurement of Resistances

Wheatstone-Bridge

$$U_d = U_0 \left(\frac{R_2}{R_1 + R_2} - \frac{R_3}{R_3 + R_x} \right)$$
$$= \frac{R_2 \cdot R_x - R_1 \cdot R_3}{(R_1 + R_2) \cdot (R_3 + R_x)} U_0$$

$$R_1 = R_2 = R_3 = R$$

Bridge Voltage


$$U_d = U_0 \left(\frac{1}{2} - \frac{R}{R + R_x} \right)$$

Dependence on R_x is nonlinear!

Sensitivity

$$E = \frac{\partial U_d}{\partial R_x} = \frac{-R}{(R + R_x)^2} U_0$$

Proportional to supply voltage

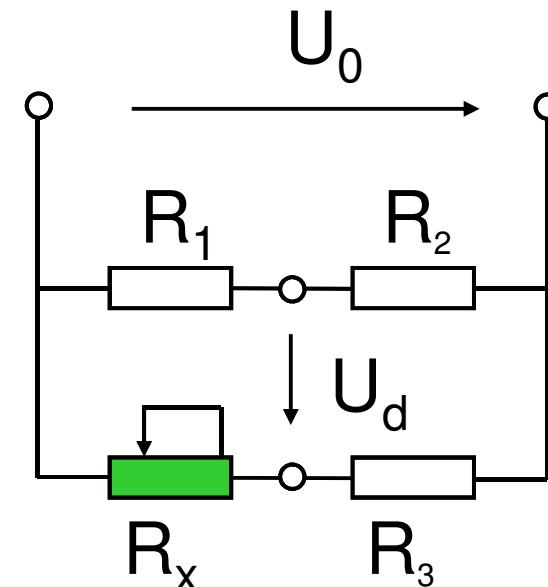

5.2 Measurement of Resistances

Wheatstone-Bridge


$$U_d = U_0 \left(\frac{R_2}{R_1 + R_2} - \frac{R_3}{R_3 + R_x} \right)$$

$$= \frac{R_2 \cdot R_x - R_1 \cdot R_3}{(R_1 + R_2) \cdot (R_3 + R_x)}$$

$$R_1 = R_2 = R_3 = R_0$$

$$R_x = R_0 + \Delta R$$
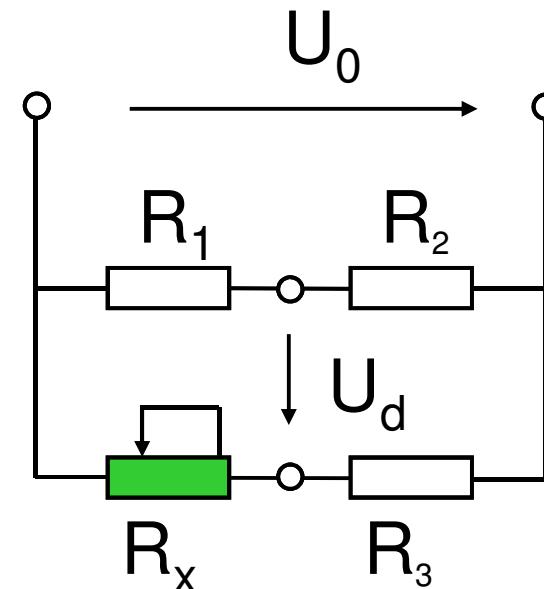
$$U_d = \frac{R_0 \cdot (R_0 + \Delta R) - R_0 \cdot R_0}{(R_0 + R_0) \cdot (R_0 + R_0 + \Delta R)} U_0$$
$$= \frac{\Delta R}{4R_0 + 2\Delta R} U_0 \approx \frac{\Delta R}{4R_0} U_0$$



$$U_d \approx \frac{\Delta R}{4R_0} U_0$$

5.2 Measurement of Resistances

1/4-, 1/2- and Fullbridge

U_d near a certain working point

$$U_d = U_0 \frac{R_2 R_3 - R_1 R_4}{(R_1 + R_2)(R_3 + R_4)}$$








For small ΔR

$$U_d = \frac{U_0}{4} \left(\frac{\Delta R_2}{R_2} - \frac{\Delta R_1}{R_1} + \frac{\Delta R_3}{R_3} - \frac{\Delta R_4}{R_4} \right)$$

-  $\rightarrow R_0 + \Delta R$
-  $\rightarrow R_0 - \Delta R$
-  $\rightarrow R_0$

[Schrüfer]

1/4-brücke

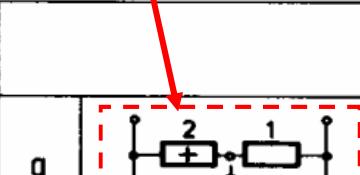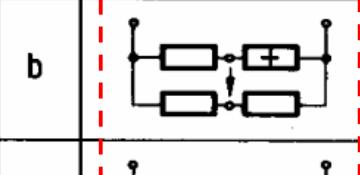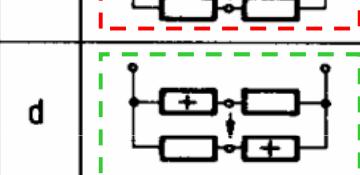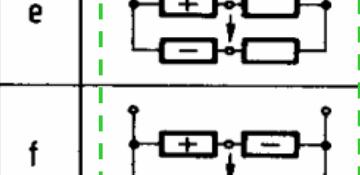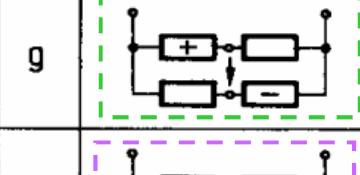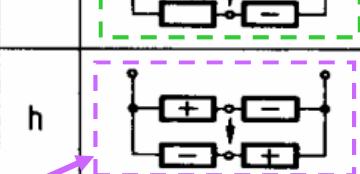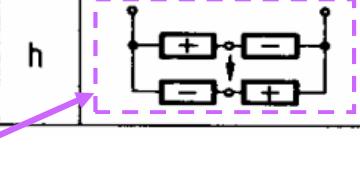
		U_0 -gespeist	I_0 -gespeist
a		$U_d \approx + \frac{U_0 \Delta R}{4 R_0}$	$U_d \approx \frac{I_0}{4} \Delta R$
b		$U_d \approx - \frac{U_0 \Delta R}{4 R_0}$	$U_d \approx - \frac{I_0}{4} \Delta R$
c		$U_d \approx - \frac{U_0 \Delta R}{4 R_0}$	$U_d \approx - \frac{I_0}{4} \Delta R$
d		$U_d \approx \frac{U_0 \Delta R}{2 R_0}$	$U_d = \frac{I_0}{2} \Delta R$
e		$U_d \approx \frac{U_0 \Delta R}{2 R_0}$	$U_d = \frac{I_0}{2} \Delta R$
f		$U_d = \frac{U_0 \Delta R}{2 R_0}$	$U_d = \frac{I_0}{2} \Delta R$
g		$U_d \approx - \frac{U_0}{4} \left(\frac{\Delta R}{R_0} \right)^2$	$U_d = - \frac{I_0}{4} \frac{\Delta R}{R_0} \Delta R$
h		$U_d = U_0 \frac{\Delta R}{R_0}$	$U_d = I_0 \Delta R$

1/2-brücke

Fullbridge

5.2 Measurement of Resistances


Fullbridge

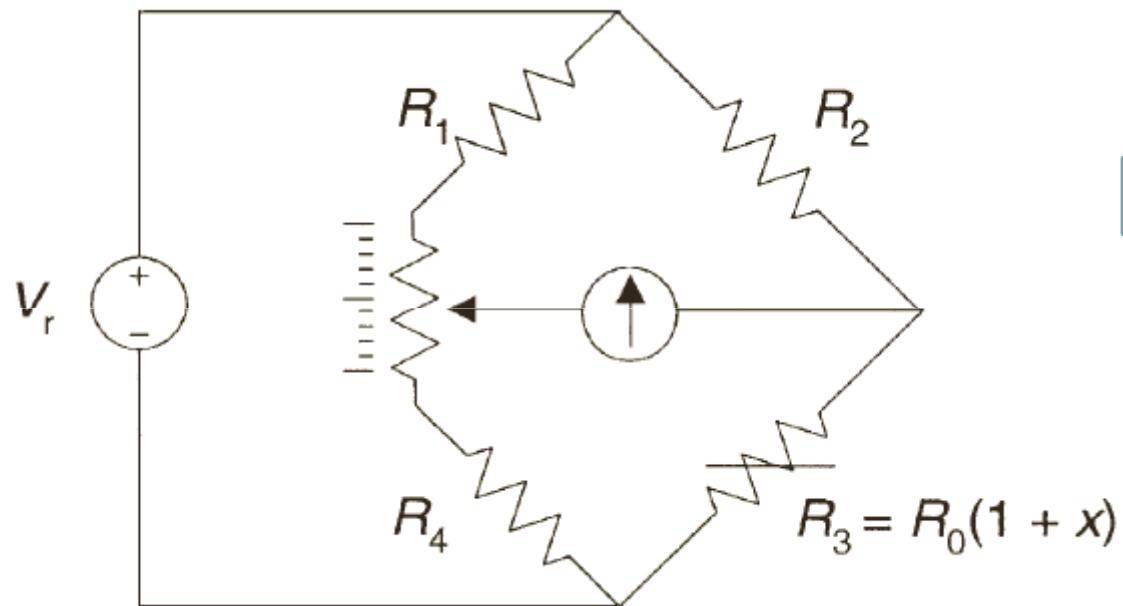

Reduction of the effect
of contact resistance

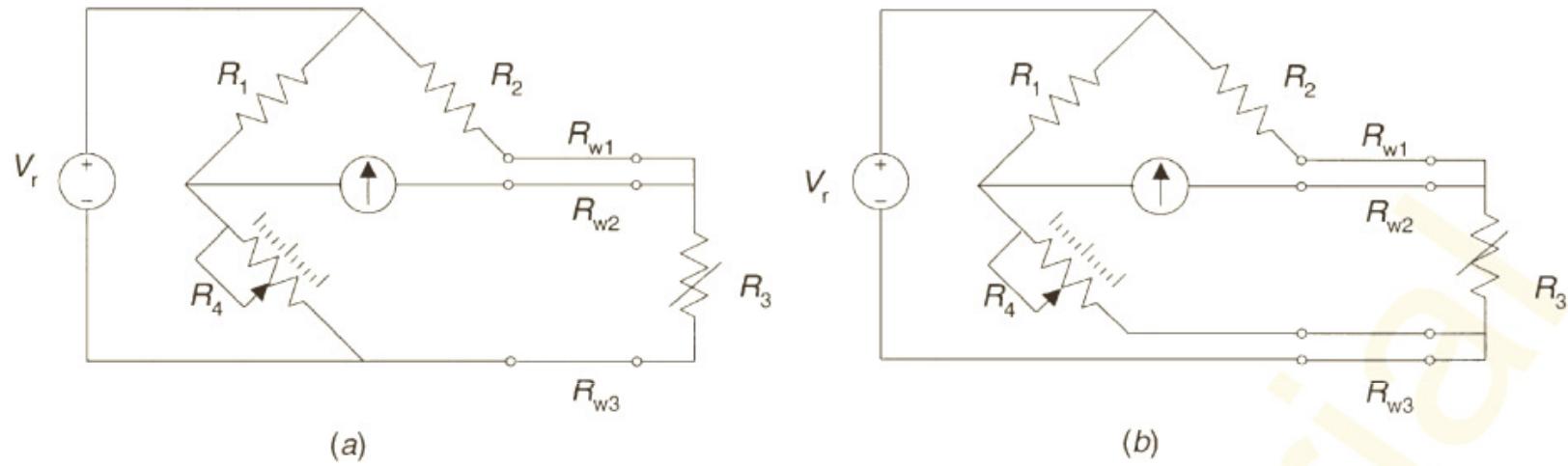5.2 Measurement of Resistances

Fullbridge with 3 wires and 4 wires contacting




Deviation: $\varepsilon = \Delta R_3 / R_3$

$$\varepsilon = \frac{R_4 R_2 / R_1 - R_3}{R_3} = \frac{R_w}{R_3} \left(1 - \frac{R_4}{R_1} \right)$$

► $R_3 \gg R_w$

5.3 Measurement of Capacitances and Inductivities

Alternating current bridge

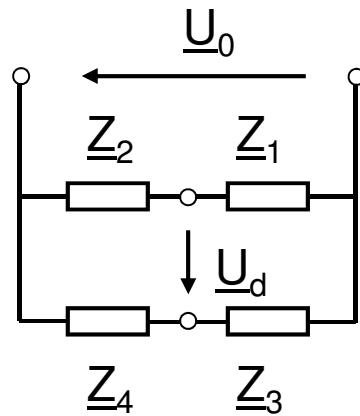

$$U_d = \left(\frac{Z_2}{Z_1 + Z_2} - \frac{Z_4}{Z_4 + Z_3} \right) \cdot U_0$$

Adjustment for $Z_1 Z_4 = Z_3 Z_2$

With $Z_k = Z_k e^{j\varphi_k}$

$$Z_1 e^{j\varphi_1} Z_4 e^{j\varphi_4} = Z_3 e^{j\varphi_3} Z_2 e^{j\varphi_2}$$

$$Z_1 Z_4 e^{j(\varphi_1 + \varphi_4)} = Z_3 Z_2 e^{j(\varphi_3 + \varphi_2)}$$

Necessary conditions for adjustment:


1. Phase condition $\varphi_1 + \varphi_4 = \varphi_3 + \varphi_2$

2. Modulus condition $Z_1 Z_4 = Z_3 Z_2$

!

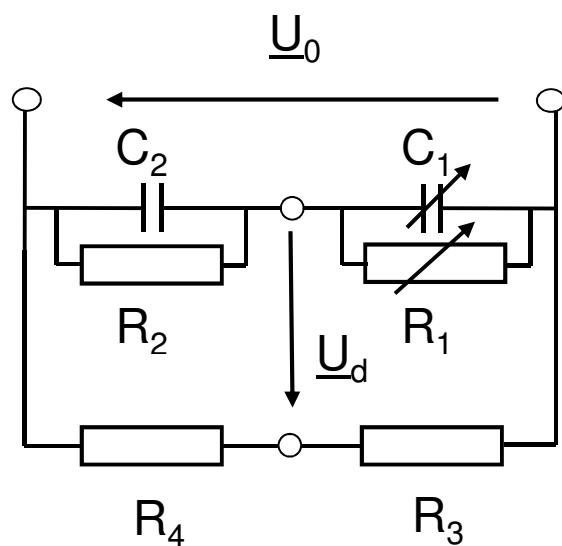5.3.1 AC-Current-Bridge

Capacitance bridge by Wien
(measurement of lossy capacitances)



R_2, C_2 are unknown

R_1, C_1 are modifiable

Condition for adjustment


$$\frac{\frac{R_2}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} R_3 = \frac{\frac{R_1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}} R_4$$

► $R_2 = \frac{R_4}{R_3} R_1$

► $C_2 = \frac{R_3}{R_4} C_1$

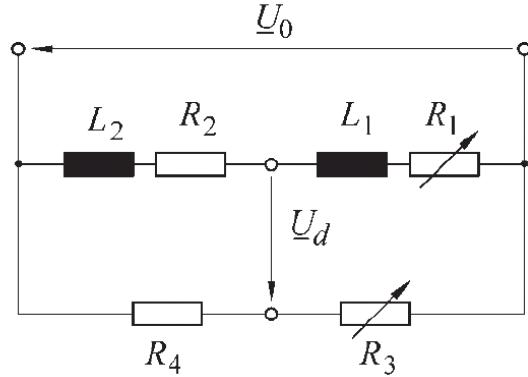5.3.1 AC-Current-Bridge

Inductivity-Bridge by Maxwell
(Measurement of lossy Inductivities)




L_2, R_2 are unknown

$$L_2 = \frac{L_1 R_4}{R_3}$$

$$R_2 = \frac{R_4}{R_3} R_1$$

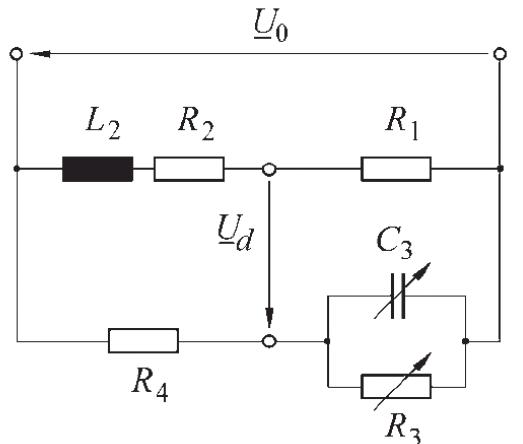Inductivity-Bridge by Maxwell-Wien
(Measurement of lossy Inductivities)




L_2, R_2 are unknown


$$L_2 = R_1 R_4 C_3$$

$$R_2 = \frac{R_1 R_4}{R_3}$$


5.3.1 AC-Current-Bridge

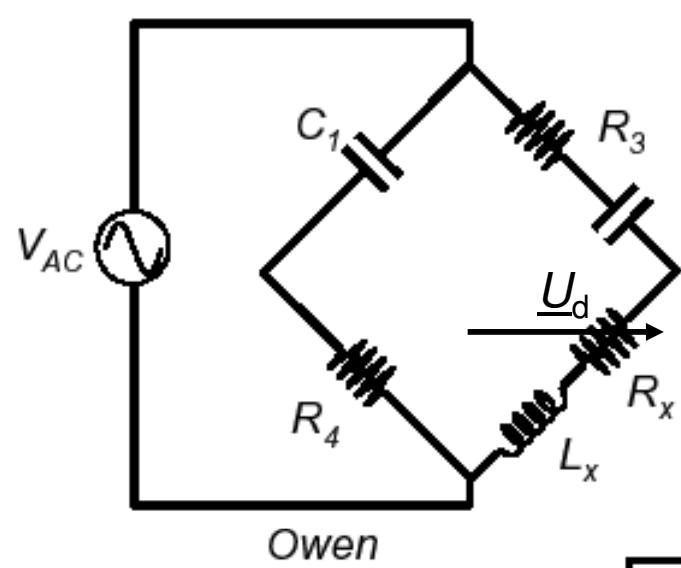

Owen

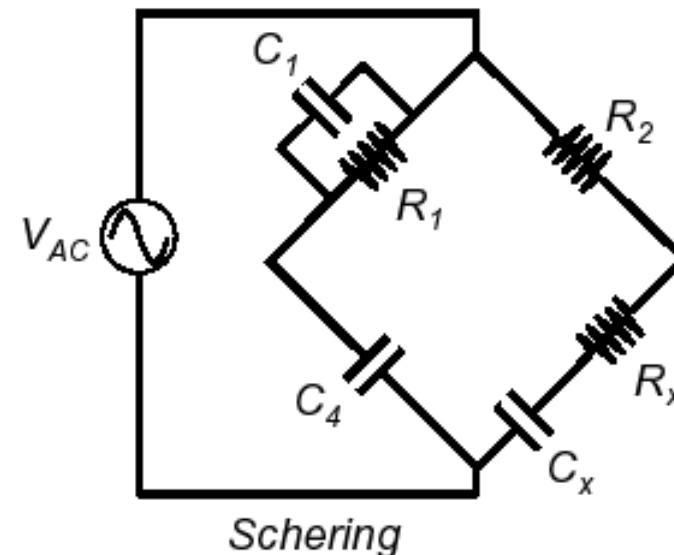


Schering

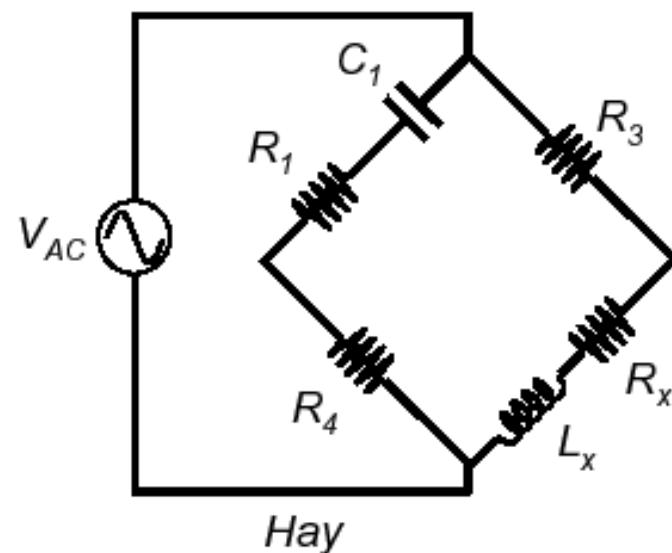

Hay


5.3.1 AC-Current-Bridge

Checking the phase condition

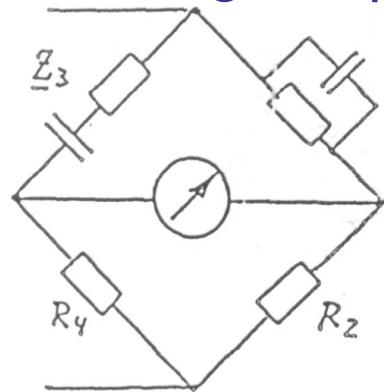


$$\begin{aligned}\varphi_3 &< 0 & \varphi &< 0 \\ \varphi_4 &= 0 & \varphi_2 &= 0\end{aligned}$$

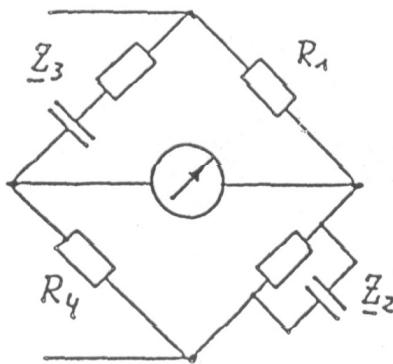$\varphi + \varphi_4 < 0$
 $\varphi_3 + \varphi_2 < 0$
 Adjustment is possible



$$\begin{aligned}\varphi_3 &< 0 & \varphi_1 &= 0 \\ \varphi_4 &= 0 & \varphi_2 &< 0\end{aligned}$$

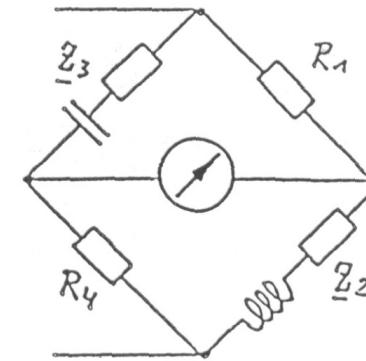$\varphi_1 + \varphi_4 = 0$
 $\varphi_3 + \varphi_2 < 0$
 Adjustment is not possible




$$\begin{aligned}\varphi_3 &< 0 & \varphi_1 &= 0 \\ \varphi_4 &= 0 & \varphi_2 &> 0\end{aligned}$$

$\varphi_1 + \varphi_4 = 0$
 $\varphi_3 + \varphi_2$ beliebig
 Adjustment is possible

The judgement of the **modulus condition** is in the special case necessary !

5.3.1 AC-Current-Bridge

Frequency dependence of the adjustment

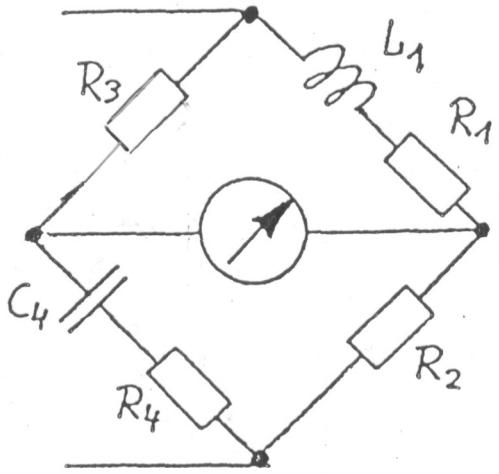


$$\underline{Z}_1 = R_1 + j \omega L_1$$

$$\underline{Z}_2 = R_2$$


$$\underline{Z}_3 = R_3$$

$$\underline{Z}_4 = R_4 - j \frac{1}{\omega C_4}$$
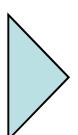
$$\underline{Z}_1 \underline{Z}_4 = \underline{Z}_3 \underline{Z}_2$$


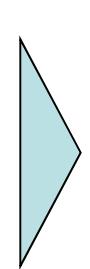
$$(R_1 + j\omega L_1) \left(R_4 - j \frac{1}{\omega C_4} \right) = R_3 R_2$$




$$R_1 R_4 + \frac{L_1}{C_4} = R_3 R_2$$

$$\frac{R_1}{\omega C_4} = \omega L_1 R_4$$

Frequency dependent
adjustment

5.3.1 AC-Current-Bridge

Frequency dependence of the adjustment

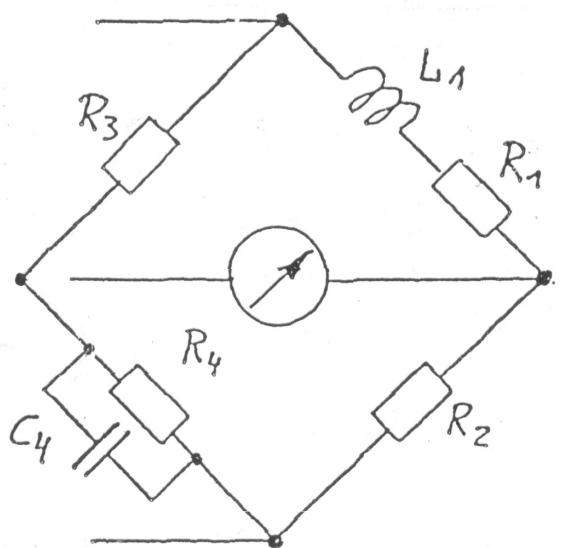


$$\underline{Z}_1 = R_1 + j \omega L_1$$

$$\underline{Z}_2 = R_2$$

$$\underline{Z}_3 = R_3$$

$$\underline{Z}_4 = \frac{1}{\frac{1}{R_4} + j\omega C_4}$$
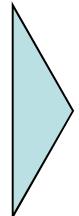
$$\underline{Z}_1 \underline{Z}_4 = \underline{Z}_3 \underline{Z}_2$$





$$R_3 R_2 = R_1 R_4$$

$$C_4 = \frac{L_1}{R_2 R_3}$$

Frequency independent adjustment!

5.3.2 Measurement with Oscillators

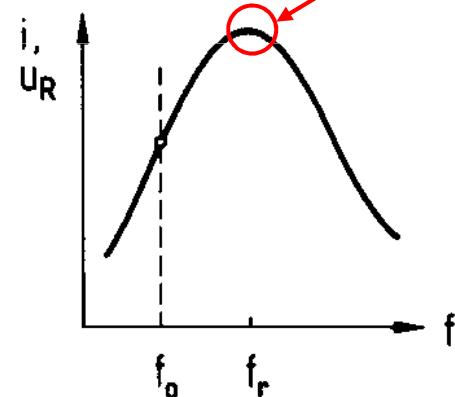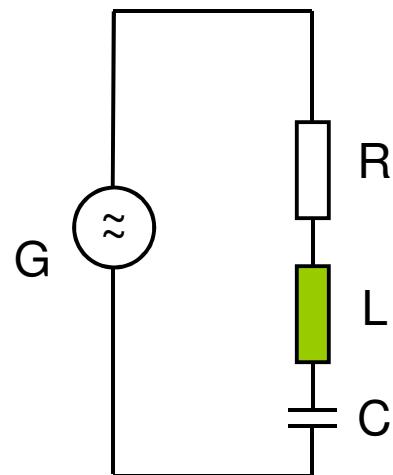

$$Z = R + jX = R + j\left(\omega L - \frac{1}{\omega C}\right)$$


Resonance frequency:

$$\omega_r L = \frac{1}{\omega_r C}$$

$$f_r = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

→ L or C measurement

Example

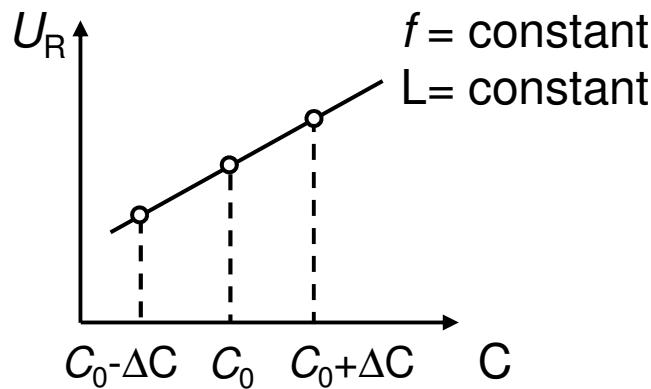


5.3.3 Charge-Transfer Method for Measurement of Capacitances

Signal preprocessing for capacitive sensors, which are suitable for monolithic Integration!

S_1 closed
→ C_x is charged to U_r

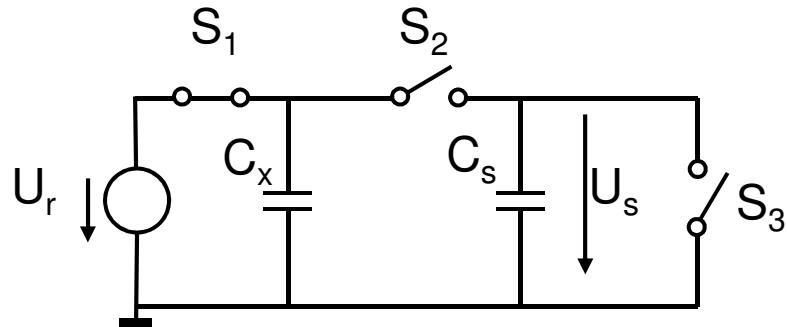S_1 opened and S_2 closed
→ C_s is charged to U_s




$$C_x \ll C_s$$

$$U_s = U_r \cdot \frac{C_x}{C_x + C_s} \approx U_r \cdot \frac{C_x}{C_s}$$

$$C_x = C_s \cdot \frac{U_s}{U_r}$$

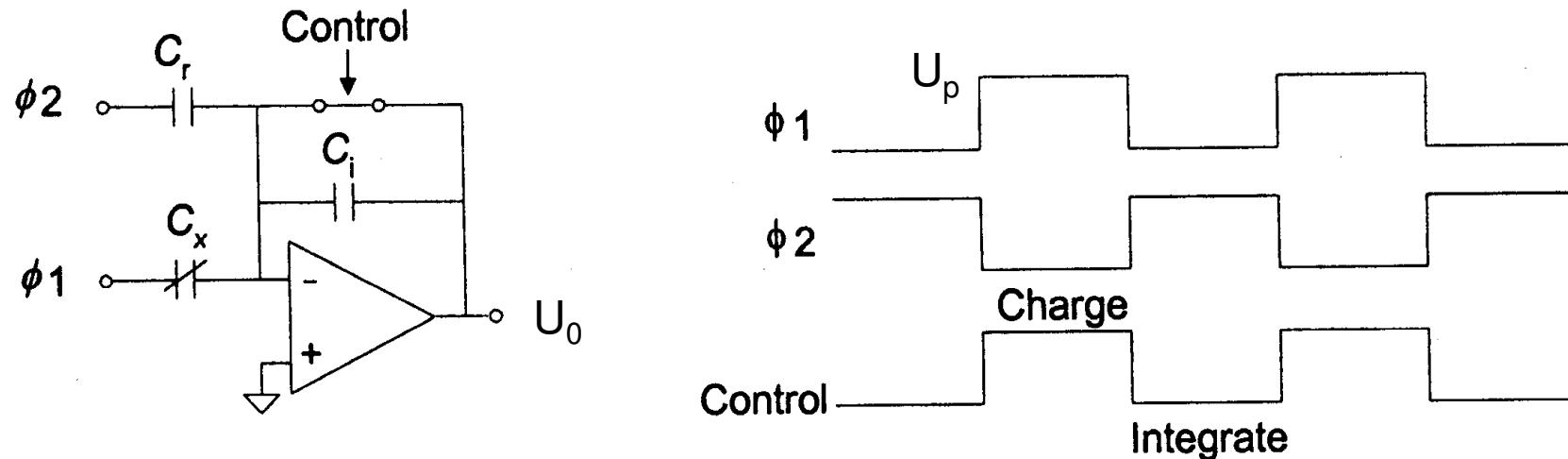5.3.3 Charge-Transfer Method for Measurement of Capacitances



Voltages Φ_1 und Φ_2 are switched together with the Relay “Control”

During Φ_1 is switched on U_p :

- Relay “Control” is closed
- The (-)-Input of the OPV is on ground
- The capacitance C_x is loaded

During Φ_2 is switched on U_p :

- The Relay “Control” is opened
- It flows a current from C_x over C_i


$$U_0 = U_p \cdot \frac{C_x - C_r}{C_i}$$

5.3.3 Power Measurement Method

$$u_1 = \hat{u}_1 \sin(\omega t + \varphi)$$

φ selectable

$$u_0 = \hat{u}_0 \sin(\omega t)$$

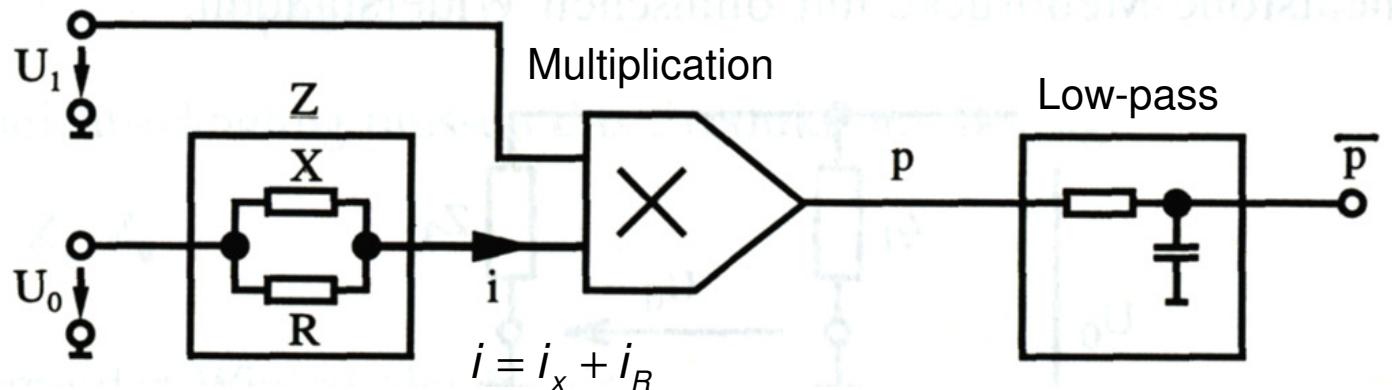

Case 1: $\varphi = 0^\circ$

$$\begin{aligned} p &= \left\{ \frac{\hat{u}_0}{R} \sin(\omega t) + \hat{u}_0 \omega C \cos(\omega t) \right\} \hat{u}_1 \sin(\omega t) \\ &= \frac{\hat{u}_1 \hat{u}_0}{R} \sin^2(\omega t) + \hat{u}_0 \hat{u}_1 \omega C \cos(\omega t) \sin(\omega t) \\ &= \frac{\hat{u}_1 \hat{u}_0}{2R} - \frac{\hat{u}_1 \hat{u}_0}{2R} \cos(2\omega t) + \frac{\hat{u}_0 \hat{u}_1}{2} \omega C \sin(2\omega t) \end{aligned}$$

$$\boxed{\bar{p} = \frac{1}{T} \int_0^T p_w(t) dt = \frac{\hat{u}_0 \hat{u}_1}{2R}}$$

$$\begin{aligned} \sin(x)\cos(y) &= \frac{1}{2}(\sin(x-y) + \sin(x+y)) \\ \sin^2(x) &= \frac{1}{2}(1 - \cos(2x)) \end{aligned}$$


Measurement of active power
 $\varphi = 0^\circ \quad \bar{p}_w = \frac{\hat{u}_0 \hat{u}_1}{2R} \quad \text{R}$

5.3.3 Power Measurement Method

$$u_1 = \hat{u}_1 \sin(\omega t + \varphi)$$

φ selectable

$$u_0 = \hat{u}_0 \sin(\omega t)$$

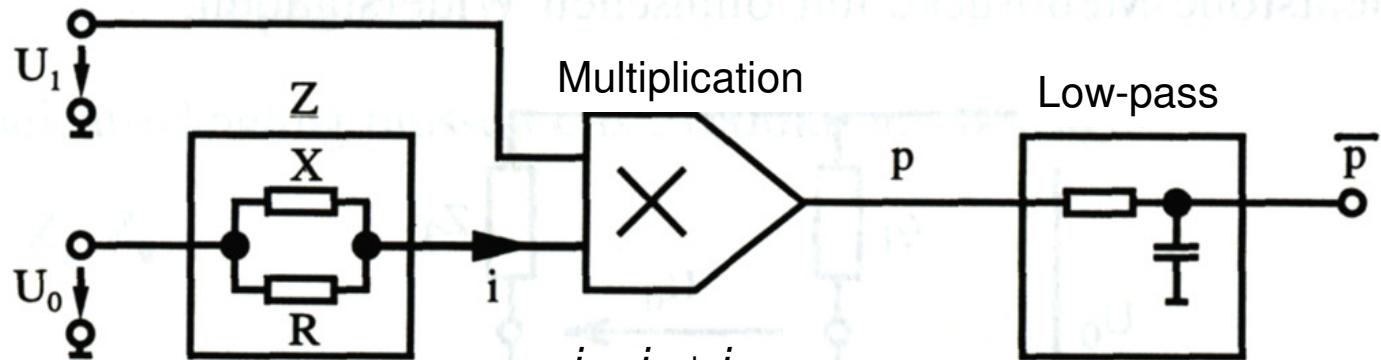

Case 2: $\varphi = 90^\circ$

$$p = \left\{ \frac{\hat{u}_0}{R} \sin(\omega t) + \hat{u}_0 \omega C \cos(\omega t) \right\} \hat{u}_1 \cos(\omega t)$$

$$= \frac{\hat{u}_1 \hat{u}_0}{R} \sin(\omega t) \cos(\omega t) + \hat{u}_0 \hat{u}_1 \omega C \cos^2(\omega t)$$

$$= \frac{\hat{u}_1 \hat{u}_0}{2R} \sin(2\omega t) + \frac{\hat{u}_0 \hat{u}_1}{2} \omega C (1 + \cos(2\omega t))$$

$$\sin(x)\cos(y) = \frac{1}{2}(\sin(x-y) + \sin(x+y))$$

$$\sin^2(x) = \frac{1}{2}(1 - \cos(2x))$$

$$\cos^2(x) = \frac{1}{2}(1 + \cos(2x))$$

$$\bar{p} = \frac{1}{T} \int_0^T p_w(t) dt = \frac{\hat{u}_0 \hat{u}_1}{2} \omega C$$

Measurement of the idle power

$$\varphi = 90^\circ \quad \bar{p}_B = \omega C \frac{\hat{u}_0 \hat{u}_1}{2}$$




5.4 Computer-based Data Acquisition-Overview

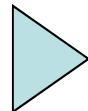Problem



Manual transfer of the measurement results



- Processing?
- Saving?
- Transfer?

Solution: Computer-based Data Acquisition


Advantages

- Automation
- Fast Acquisition
(Nyquist-Criterion)
- Fast Data Transfer
- Big Memory
- Signal Processing

Concepts

- Connection to a PC
→ Bus Systems
- Integration in a PC
→ Plug-in Cards

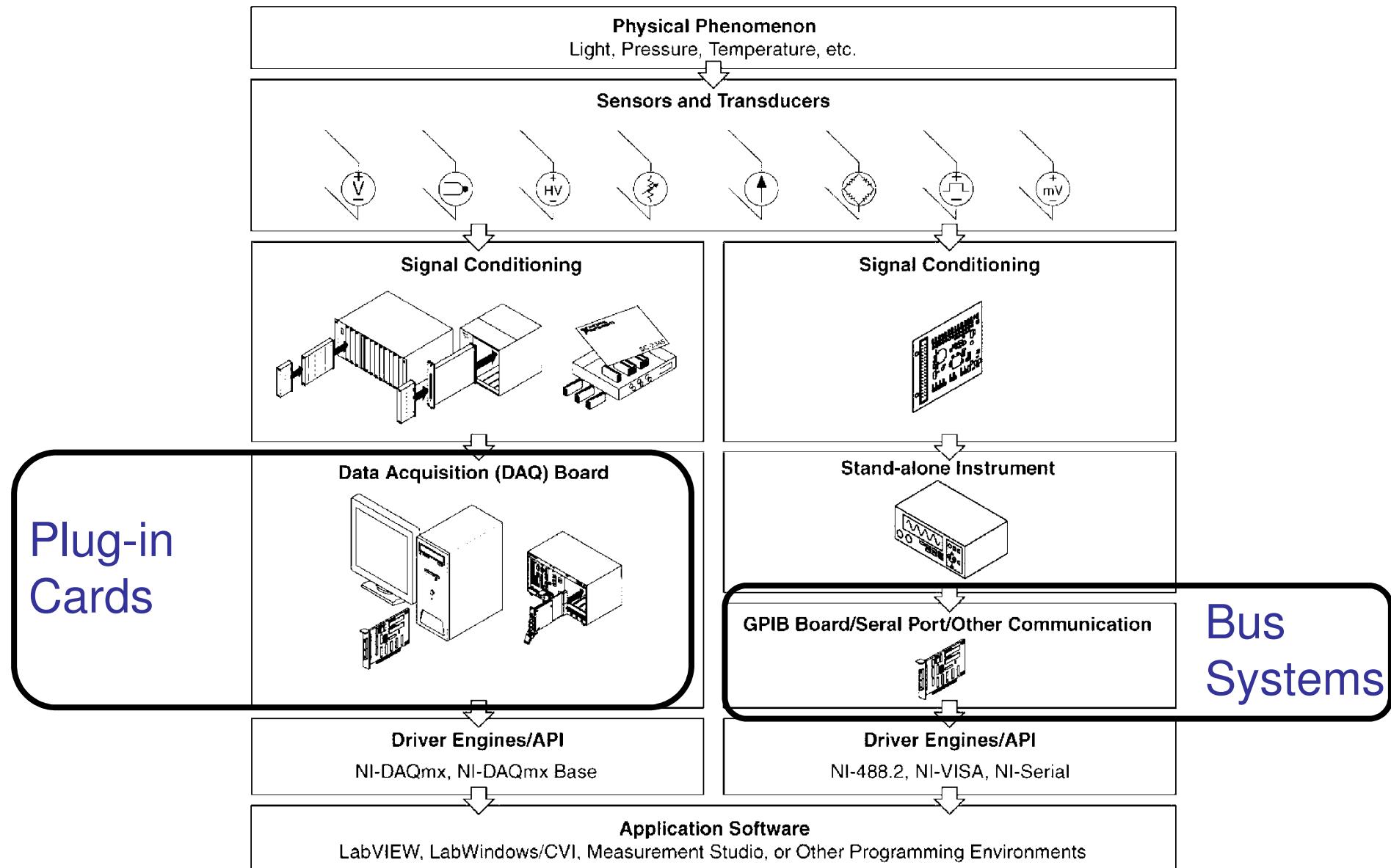5.4 Computer-based Data Acquisition-Overview



5.4 Computer-based Data Acquisition Bus Systems

Advantages

- Combination of inhomogeneous Architectures
- Special Measurement Devices can be used

Often used communication networks

- GPIB
- RS232, RS xyz
- CAN
- Ethernet
- USB

Example: GPIB
parallel 8-Bit, until 15 devices
Device has a coded Address (1-15)



5.4 Computer-based Data Acquisition Bus Systems – Use over Driver Libraries

Use of GPIB in MATLAB

```
voltmeter = gpib('ni',0,1);  
fopen(voltmeter)  
fprintf(voltmeter,'measure:volt')
```

Start a Measurement

```
fprintf(voltmeter,,read?)  
data = fscanf(voltmeter)  
fclose(voltmeter)
```

Interrogation of the Measurement Value

Read-out of the data buffer

Further commands according to the instruction set of the measurement Device

Command	Description
:CONFigure:<function>	Places the Model 2000 in a “one-shot” measurement mode for the specified function.
:FETCh?	Requests the latest reading without triggering.
:READ?	Performs an :ABORT, :INITiate, and a :FETCh?.
MEASure[:<function>]?	Performs an :ABORT, :CONFigure:<function>, and a :READ?.

:CONFigure:<function>

<function> =	CURRent:AC	AC current
	CURRent[:DC]	DC current
	VOLTage:AC	AC voltage
	VOLTage[:DC]	DC voltage
	RESistance	2-wire resistance
	FRESistance	4-wire resistance
	PERiod	Period
	FREQUency	Frequency
	TEMPerature	Temperature
	DIODE	Diode testing
	CONTinuity	Continuity test

5.4 Computer-based Data Acquisition Plug-in Cards


Advantages

- Low Costs
- Universal Use



Applications:

- Multi functional Data Acquisition
- Signal Generators
- Image Acquisition and Processing

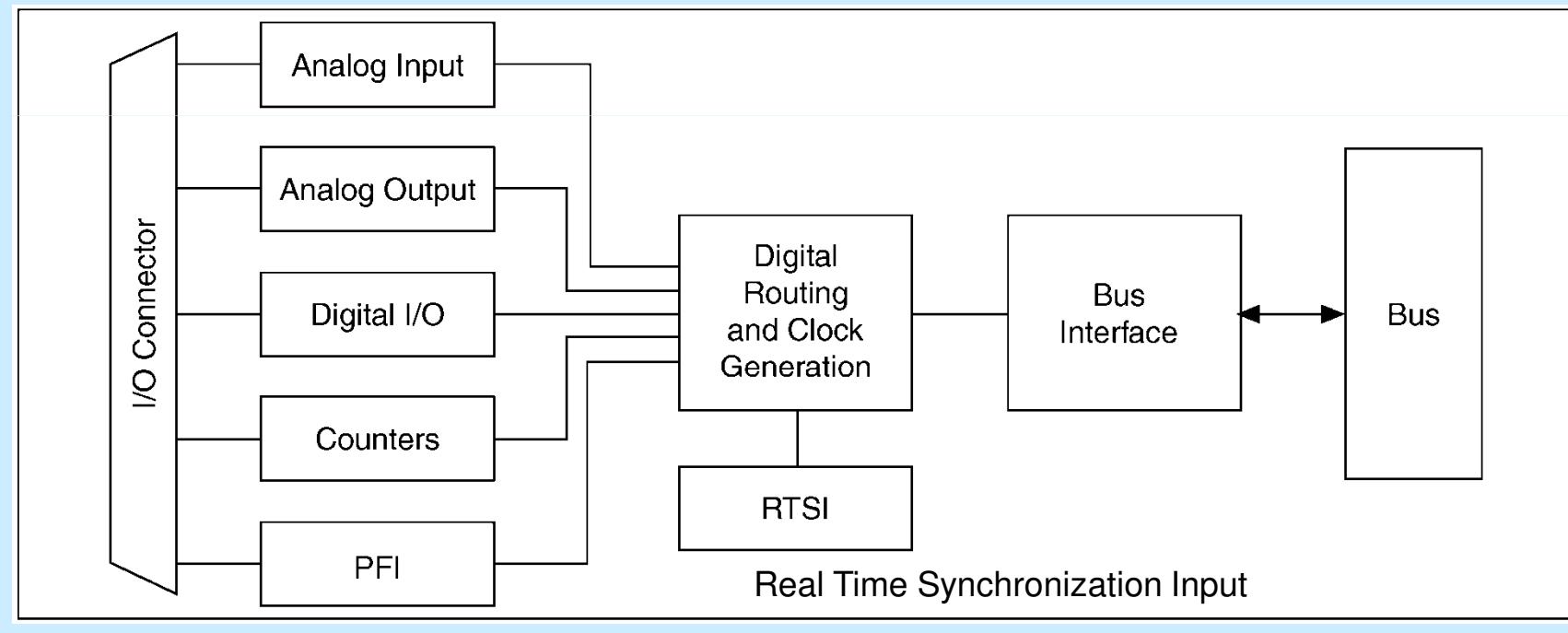Example: National Instruments M-Series Multi Functional Plug-in Card



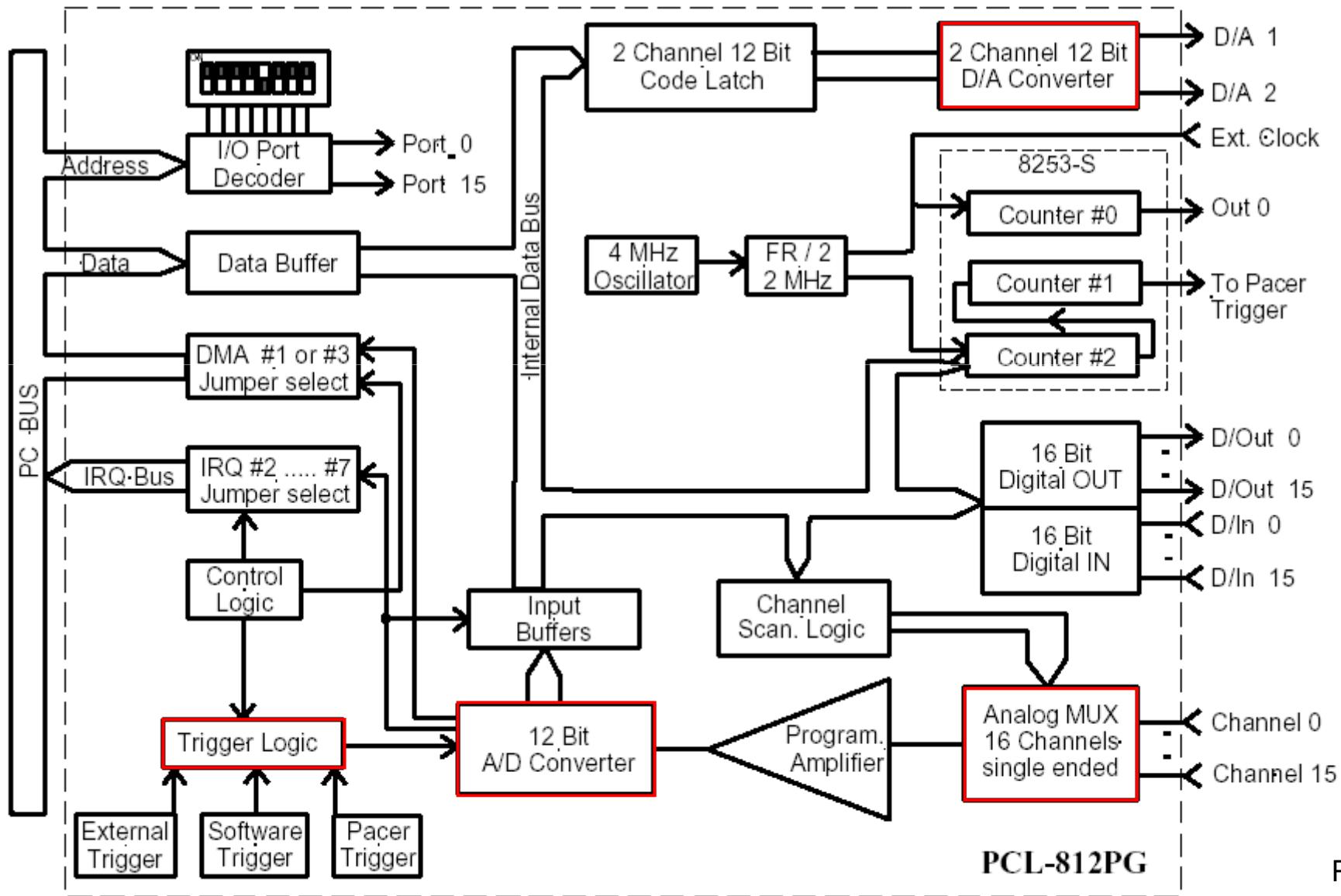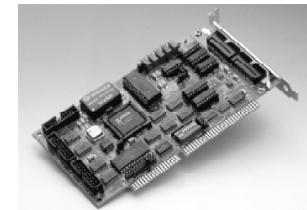5.4 Computer-based Data Acquisition Example of a Plug-in Card



5.4 Computer-based Data Acquisition Plug-in Cards— Use of Driver Library


Use in C

```
#include <NIDAQmx.h> ← Function library of the card
...
DAQmxCreateTask(taskHandle); ← Pointer on the data sector
...
DAQmxStartTask(taskHandle);
...
DAQmxReadAnalog(taskHandle,...,data); ← Depositing the data in
...
DAQmxStopTask(taskHandle); a variable
```

5.4 Computer-based Data Acquisition Plug-in Cards— Use of Driver Library

Use in LabView

Errors-Warnings

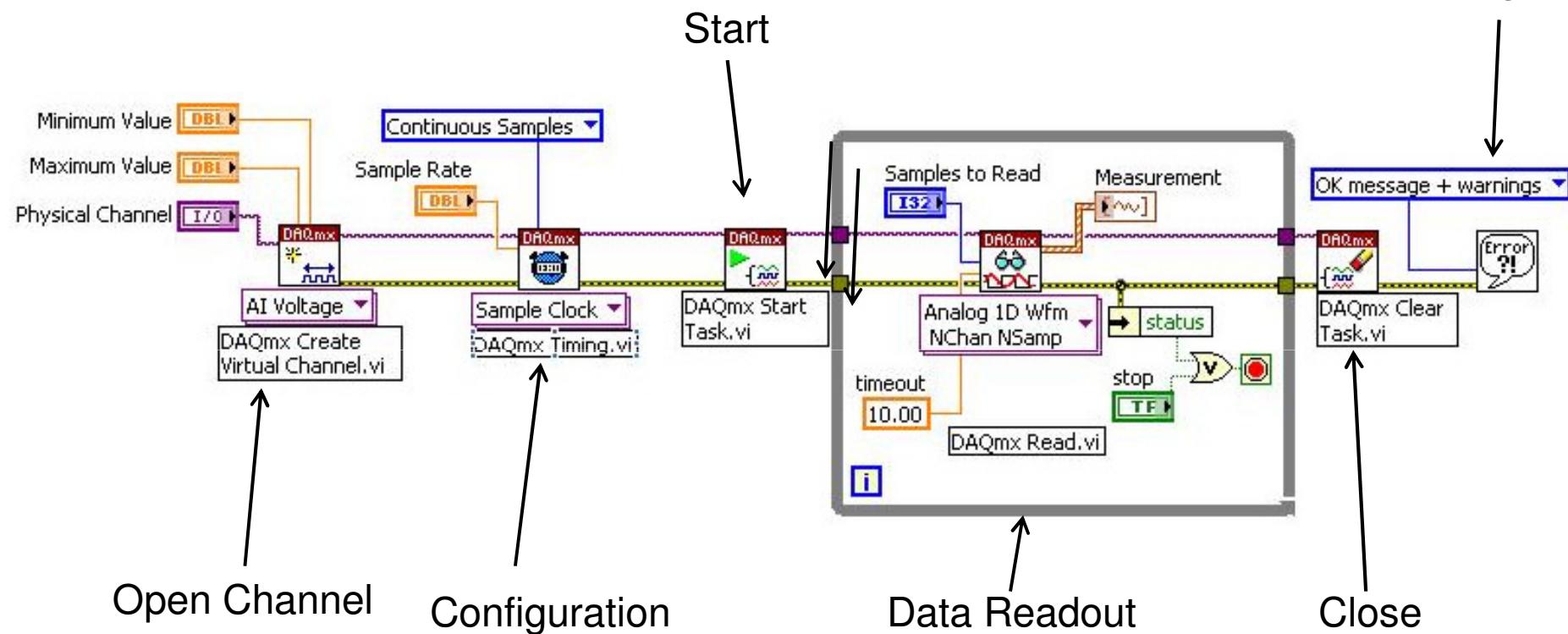

5.4 Computer-based Data Acquisition Evaluation Software

Examples for Software

- MATLAB
- C / C++
- Visual Basic
- Excel

} Use of hardware over driver
bibliothek

Further Software for Data Evaluation

- Maple
- Mathematica
- Maxima (open source)
- Scilab (open source)
- Octave (open source)

} Symbolic
} Numeric

Example: Differentiation in
Maxima

```
(%i1) diff(x^3,x,2);  
(%o1) 6 x
```

Example Statistic in Octave

```
octave-3.0.1.exe:3> x=rand(1,5)  
x =  
0.12758 0.80826 0.99206 0.82528 0.78898  
octave-3.0.1.exe:4> std(x)  
ans = 0.33464
```

5.4 Computer-based Data Acquisition Special Software

Softwarepa- ket	Lieferant	Merkmale
DASYLab	Datalog Mönchengladbach	Grafisch interaktives Paket auf Windows-Basis Schaltpläne für Meß- und Steueraufgaben, Interaktive Erstellung Funktionsmodule für Messen, Steuern, Analyse Visualisierung am Bildschirm während des Ablaufs Treiber für gängige Meßwerterfassungskarten Übernahme von Ergebnisse in andere Windowsprogramme
ARGUS / NT	Sorcus Düsseldorf	Echtzeitfähige Standardsoftware zum Messen, Prüfen, Überwachen unter Windows NT, 95 und 98 Umfangreiche Meß-, Auswerte- und Analysefunktionen
LABVIEW	National Instruments	Grafische Programmiersprache auf der Basis von C zum Aufbau von Meßwert- erfassungs- und Steuerungssystemen mit grafischer Bedienungsoberfläche
DIADEM	Gesellschaft für Strukturanalyse GfS Aachen	PC-Werkstatt unter Windows mit Geräten aus Software zur one-line und off-line Bearbeitung technischer Daten Konzeptionell mit DASYLab und ARGUS vergleichbar Umfangreiche Treiber-Bibliothek Autosequenzen für den automatischen Ablauf wiederkehrender Sequenzen
FlexPro	Weisang GmbH Menden	Dokumentieren, analysieren und archivieren (Windows) Datenbanken für umfangreiche Meßdateien Importfilter für unterschiedliche Datenformate Script-Sprache zur Erstellung von Formeln Darstellung in 2D-, 3-D-Diagrammen, Tabellen

VEE

Agilent

Messdatenerfassung

:


5.4 Computer-based Data Acquisition

Labview: User Interface



5.4 Computer-based Data Acquisition

Labview: Program Hierarchy

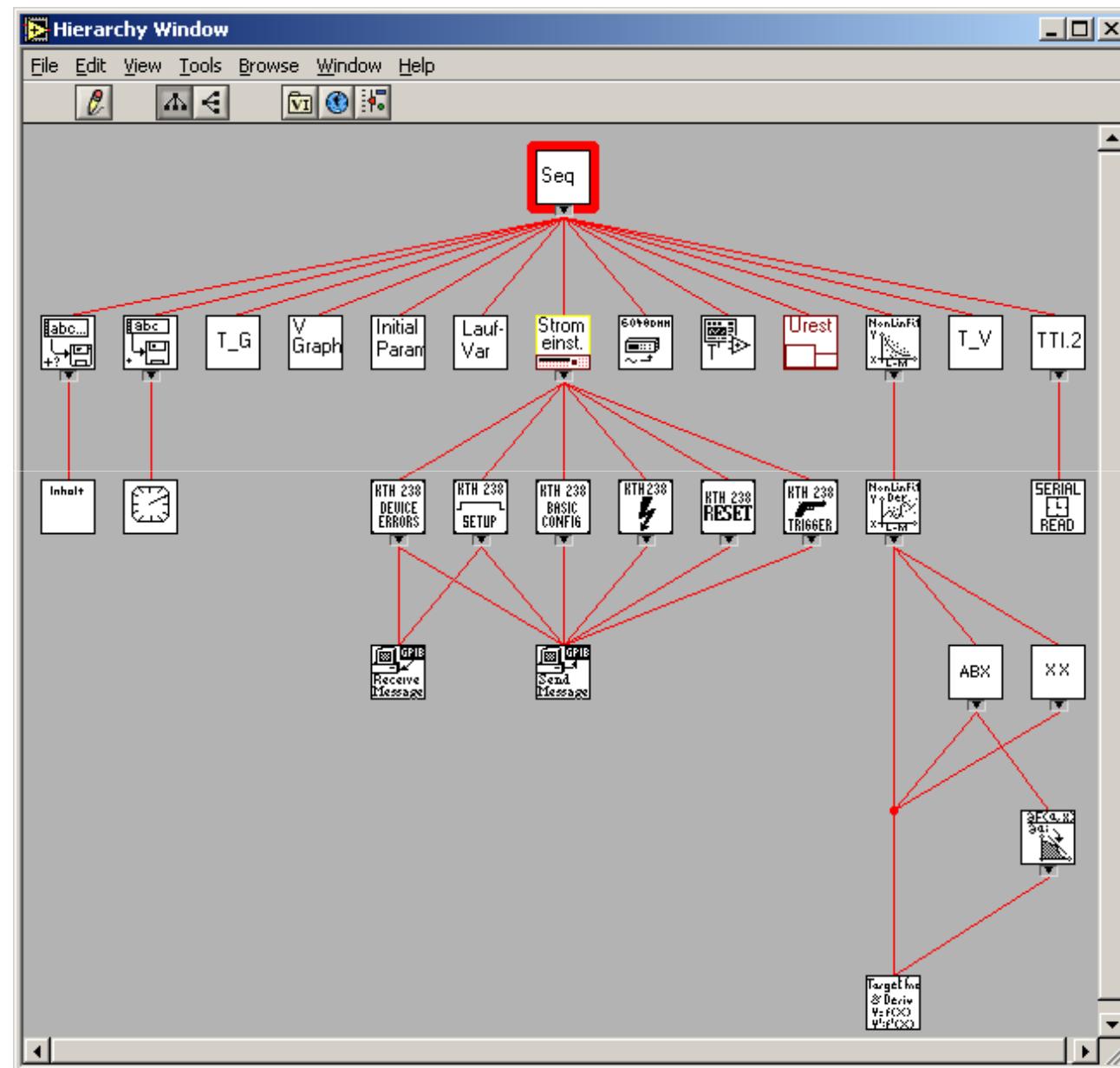

5.4 Computer-based Data Acquisition Program

